

# GMII Electrical Specification Options

## DC Specifications

**Mandatory - Communication between the transmitter and receiver can not occur at any bit rate without DC specifications.**

## AC Specifications

**OPTION 1: Use the conventional approach.**

**Specify one or two DC potentials at which all AC timing measurements are made, specify receiving register minimum setup and hold times, perhaps specify driver minimum and maximum clock to output delays and model the effect of trace and receiver input capacitance on the driver as a lumped capacitor.**

**Advantage - Simple**

**Disadvantages -**

**PCB trace length limited to avoid transmission line effects (limited to about 1.5 inches for 0.50 ns 10%-90% risetime and FR4 stripline).**

**No support for transmission line knowledgeable designers wanting to use longer traces (no assurance of adequate drive strength to insure first incident wave switching).**

**OPTION 2: Pick a topology (such as point to point),  
a minimum pcb trace impedance (such as 50 Ohms +/- 15%),  
a maximum pcb trace length and  
a termination technique (such as series/source termination) and  
specify the driver output characteristics.**

**Advantages -**

**It insures correct operation with transmission lines for one topology.**

**It permits correct operation with transmission lines whose impedance is greater than the minimum.**

**Disadvantages -**

**Unnecessarily restrictive in terms of techniques used and topologies supported.**

**OPTION 3: Specify a standard GMII receiver input equivalent circuit,  
define a “GMII Interoperability Interface” at the GMII receiver input pin,  
specify a “GMII Receiver Input Potential Template” that must be complied with at the input of  
all GMII receivers,  
specify a basic transmission line topology that all GMII drivers must support,  
let each vendor select the GMII driver characteristics and termination scheme to comply with the  
GMII Receiver Input Potential Template for the basic transmission line topology and  
allow each vendor to support other transmission line topologies subject to the requirement that  
the input signal to each GMII receiver must comply with the GMII Receiver Input Signal  
Template.**

**Advantages -**

**Insures minimum support for transmission lines.  
Allows vendors flexibility in how they support the basic topology.  
Allows vendors flexibility in supporting other transmission line topologies.**

**Disadvantages -**

**Minimal**

**Challenges**

**Model of the GMII Receiver input circuit.  
Effect of the GMII Receiver input circuit on the input potential waveform.**

# **Proposed GMII Electrical Specification Objectives**

**Implementable with either 2.5 Volt or 3.3 Volt I/O pads**

**Compatible with 10 bit SerDes electrical specifications when implemented with 3.3 Volt I/O pads**

**Support point to point connections with PCB traces up to 6 inches in length and a minimum trace impedance of 50 Ohms +/- 15%**

**Specify the AC input signal to GMII receivers.**

**Do not specify the GMII driver AC characteristics**

**Do not specify the termination technique**

**Do not preclude other GMII interconnect topologies**

## Simulations

**Frequency domain (Fourier) techniques are used which requires linear components**


**The driver model has constant output resistance.**

**This is not accurate for a driver with nonlinear output characteristics. But it is a reasonable approximation when source termination is used and the values of the series termination resistor is much greater than the driver output resistance.**


**The transmission line model used is for stripline with**

**a dc resistance of 0.1006 Ohms per inch (5 mil wide pcb trace on 1 oz. copper),  
a skin effect corner frequency of 7.42 MHz,  
a dielectric constant of 4.22 at 1.0 MHz and that decreases 0.12 per frequency decade  
a dielectric Dissipation Factor of 0.024**
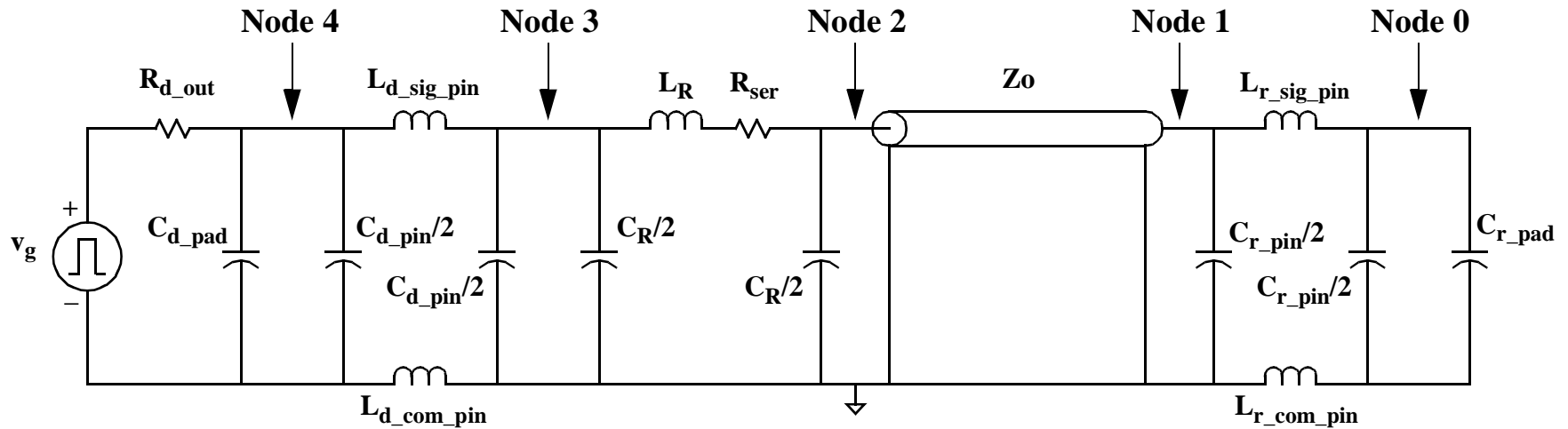
## Simulation Model - Source (Series) Termination


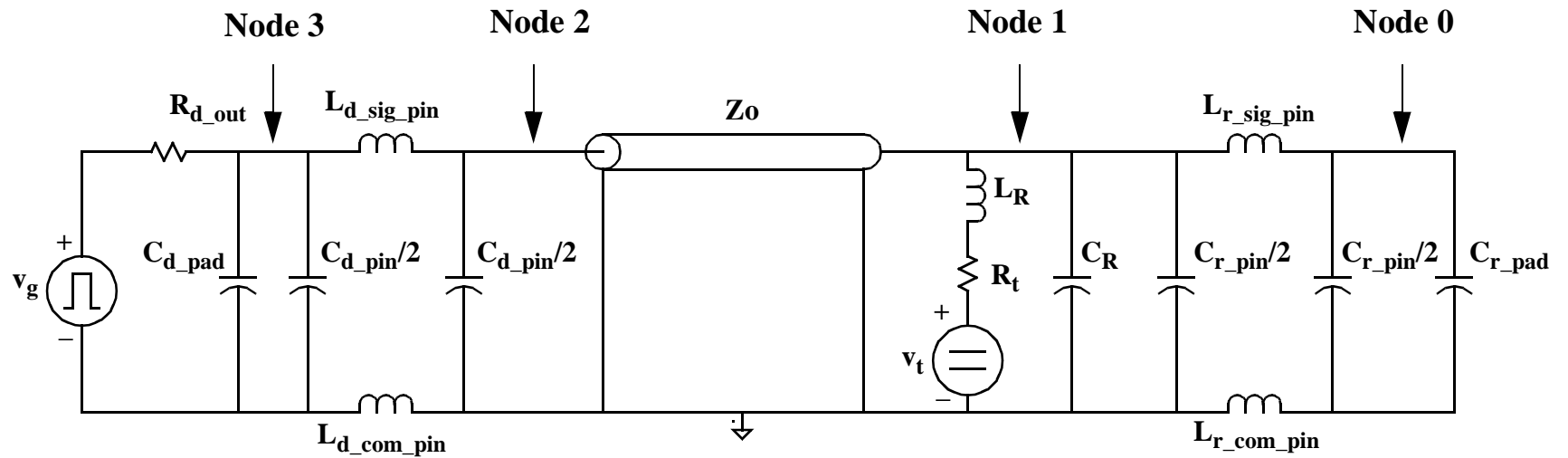
## Simulation Model - End (Parallel) Termination



## **Examples of Transmission Line behavior for**

**a driver output resistances of  $2.0 \cdot Z_0$  and  $0.5 \cdot Z_0$**

**stripline pcb trace lengths of 0.75, 1.5, 3.0 and 6.0 inches**


### **Note that**

**The output resistance of the driver functions as a mismatched source/series termination in these examples.**

**The output drive of a CMOS driver can vary at least 3:1 over supply potential, temperature and process variation.**



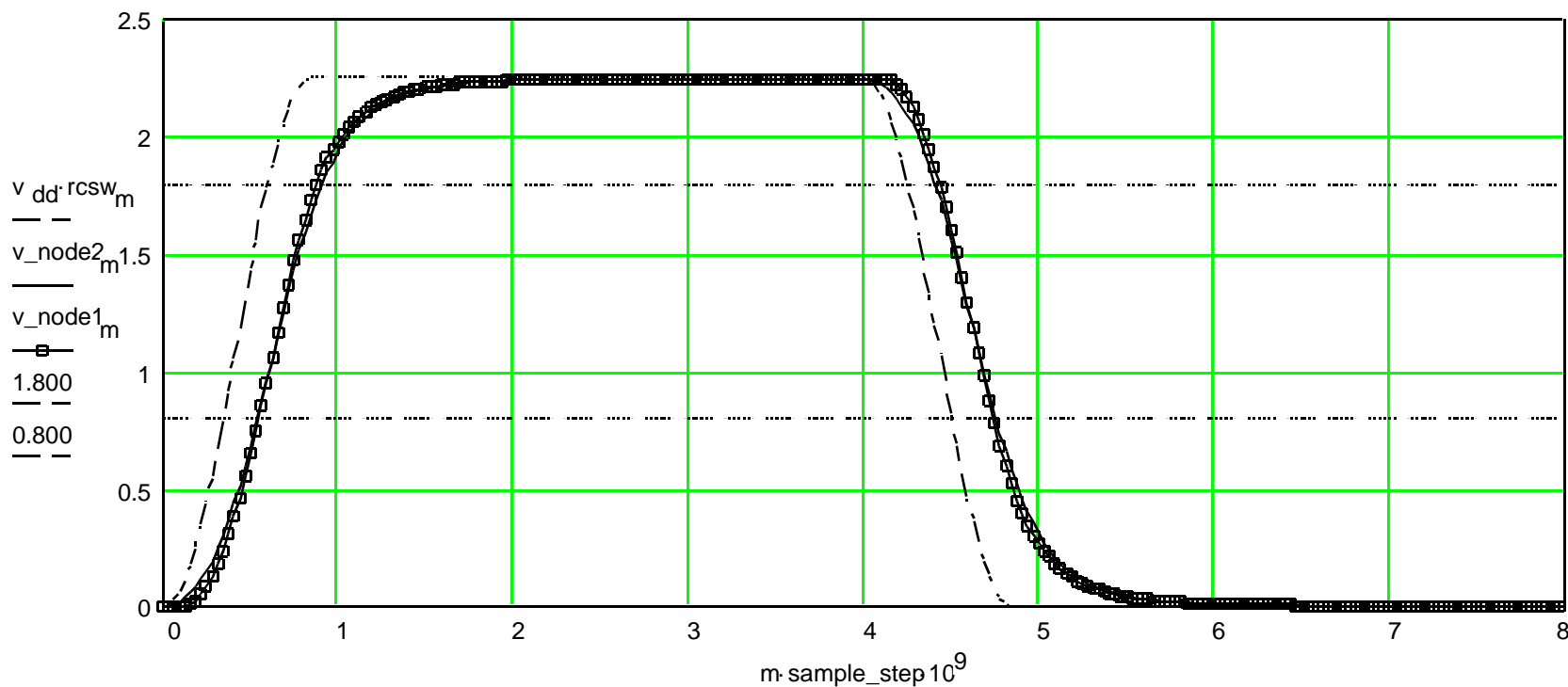
## Underdrive: $R_{d\_out} = 2 \cdot Z_o$




$v_{dd} = 2.25$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 0.75$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 100$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 0.125$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$
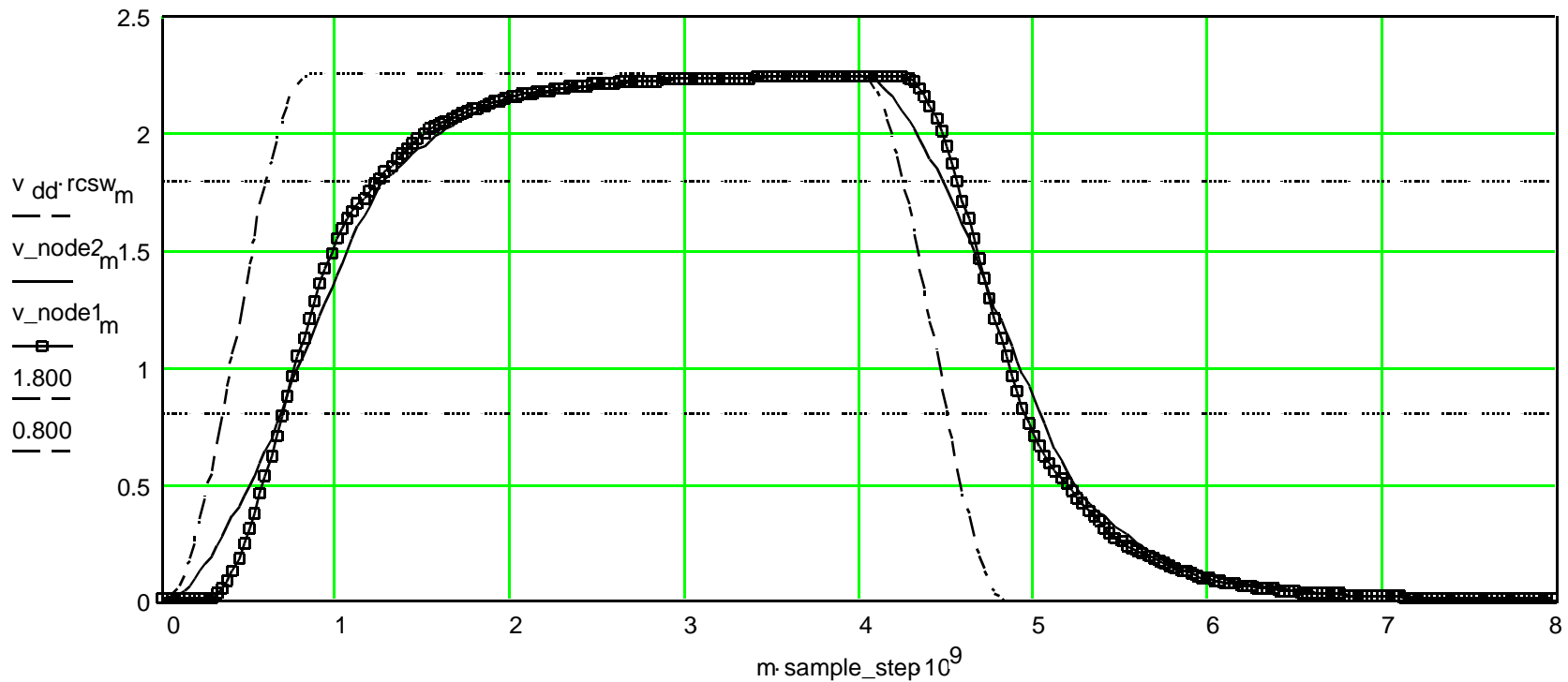
## Underdrive: $R_{d\_out} = 2 \cdot Z_o$




$v_{dd} = 2.25$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 1.5$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 100$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 0.25$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$
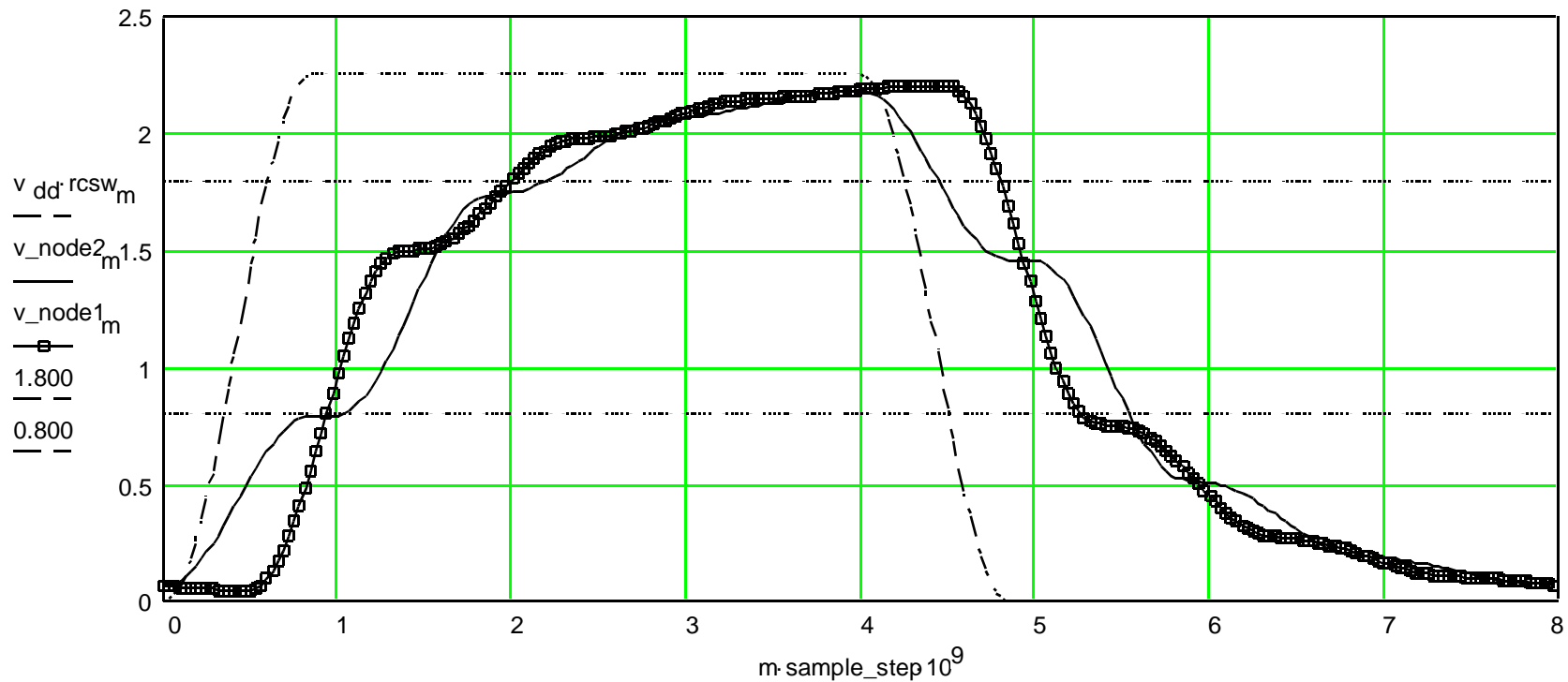
## Underdrive: $R_{d\_out} = 2 \cdot Z_o$




$v_{dd} = 2.25$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 3$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 100$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 0.5001$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$
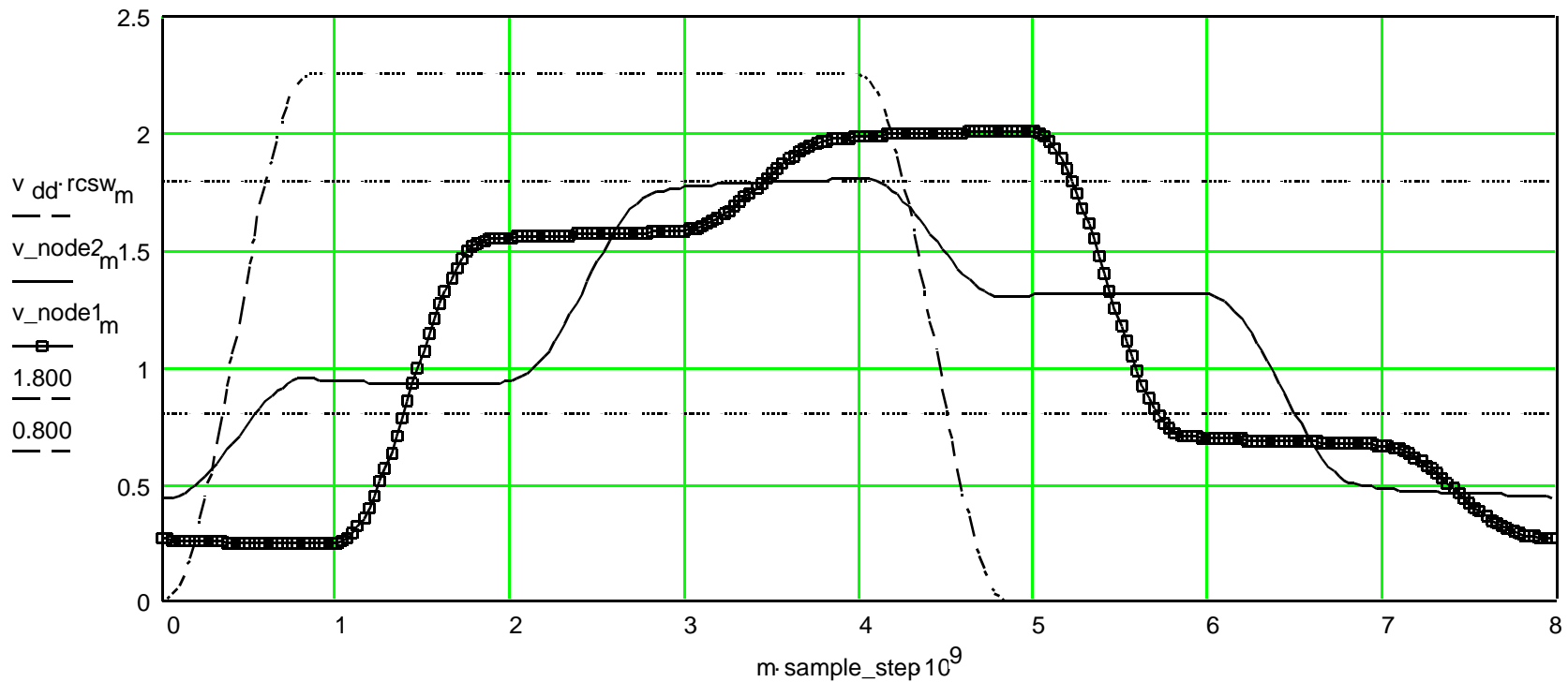
## Underdrive: $R_{d\_out} = 2 \cdot Z_o$



$v_{dd} = 2.25$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 100$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$

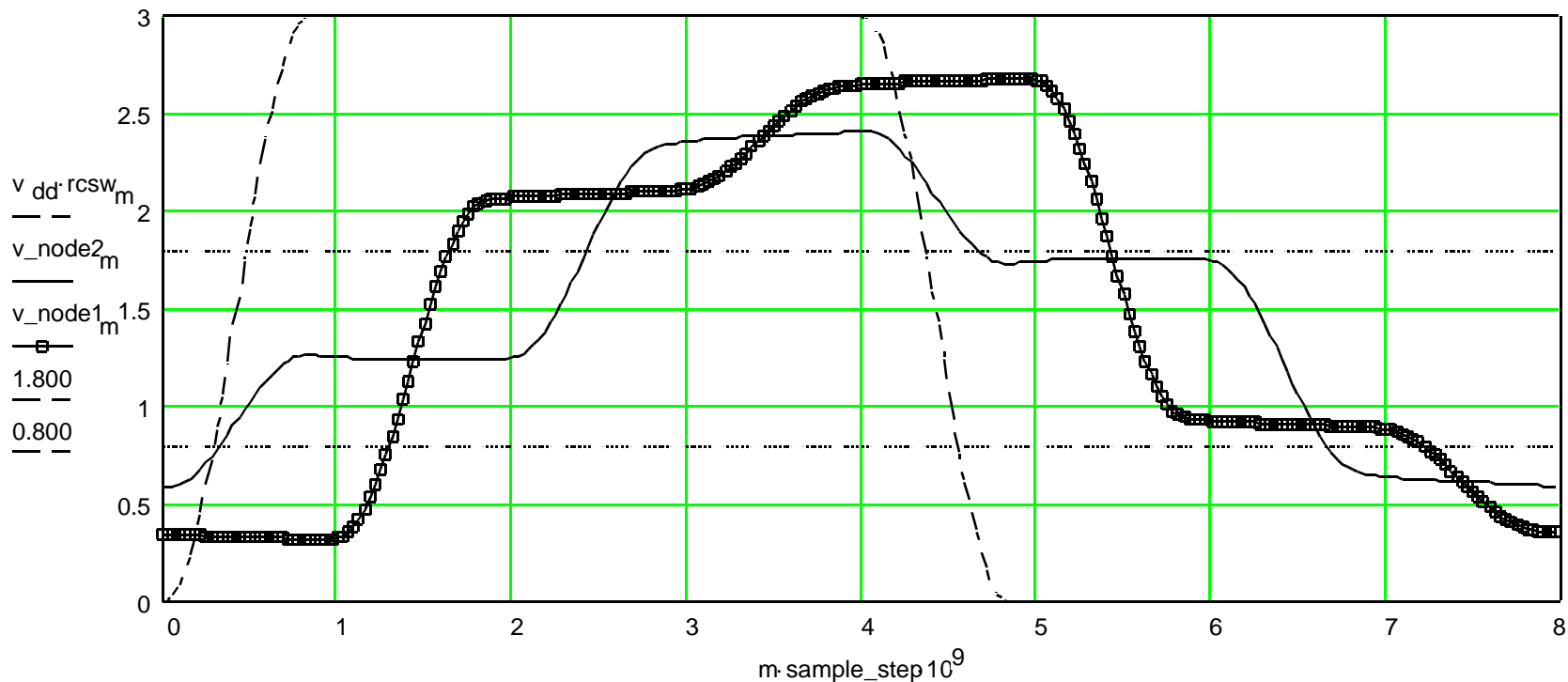
## Underdrive: $R_{d\_out} = 2 \cdot Z_o$



$v_{dd} = 3$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 100$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$


**Increasing  $V_{dd}$  solves a problem on the rising edge but creates a problem on the falling edge**

## Overdrive: $R_{d\_out} = Z_o/2$

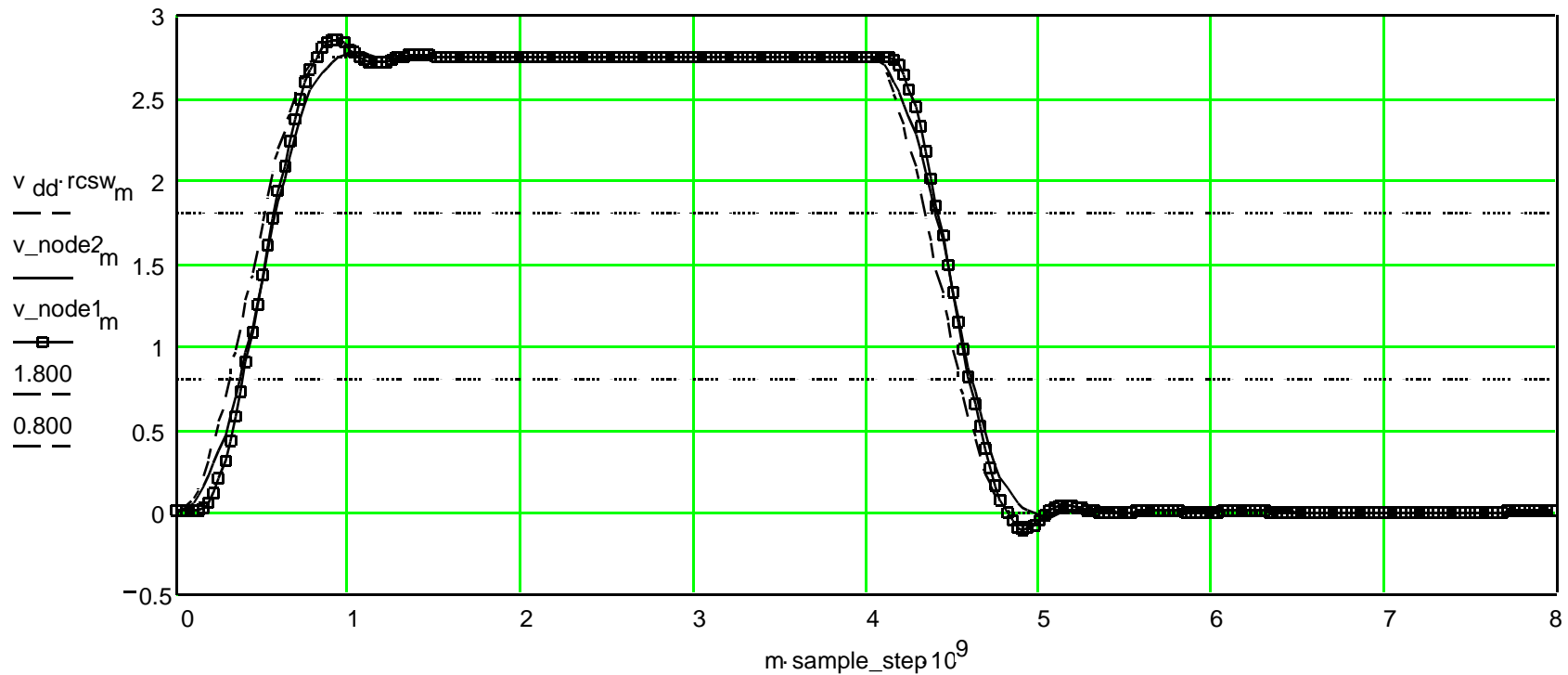


$v_{dd} = 2.75$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 0.75$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 25$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 0.125$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$

## Overdrive: $R_{d\_out} = Z_o/2$

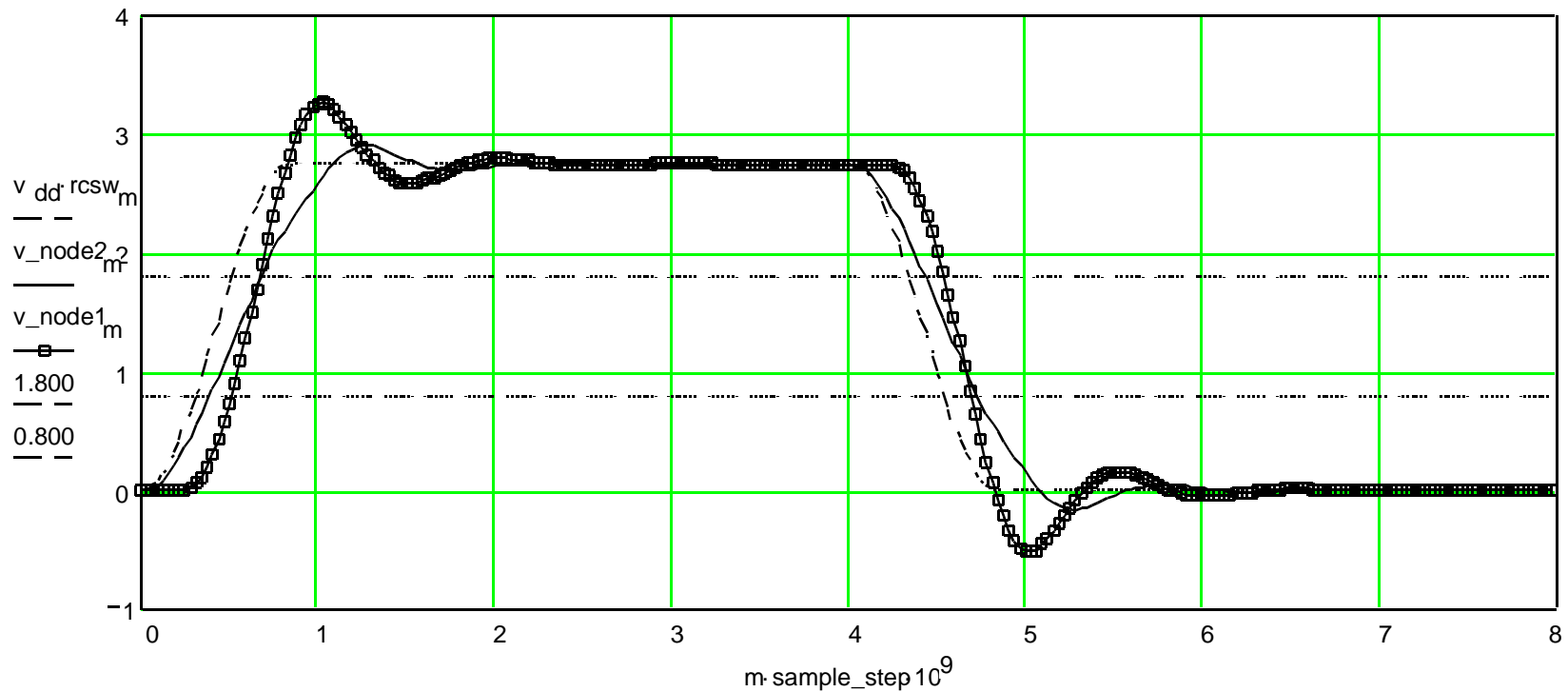

$v_{dd} = 2.75$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 1.5$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 25$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 0.25$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$


## Overdrive: $R_{d\_out} = Z_o/2$

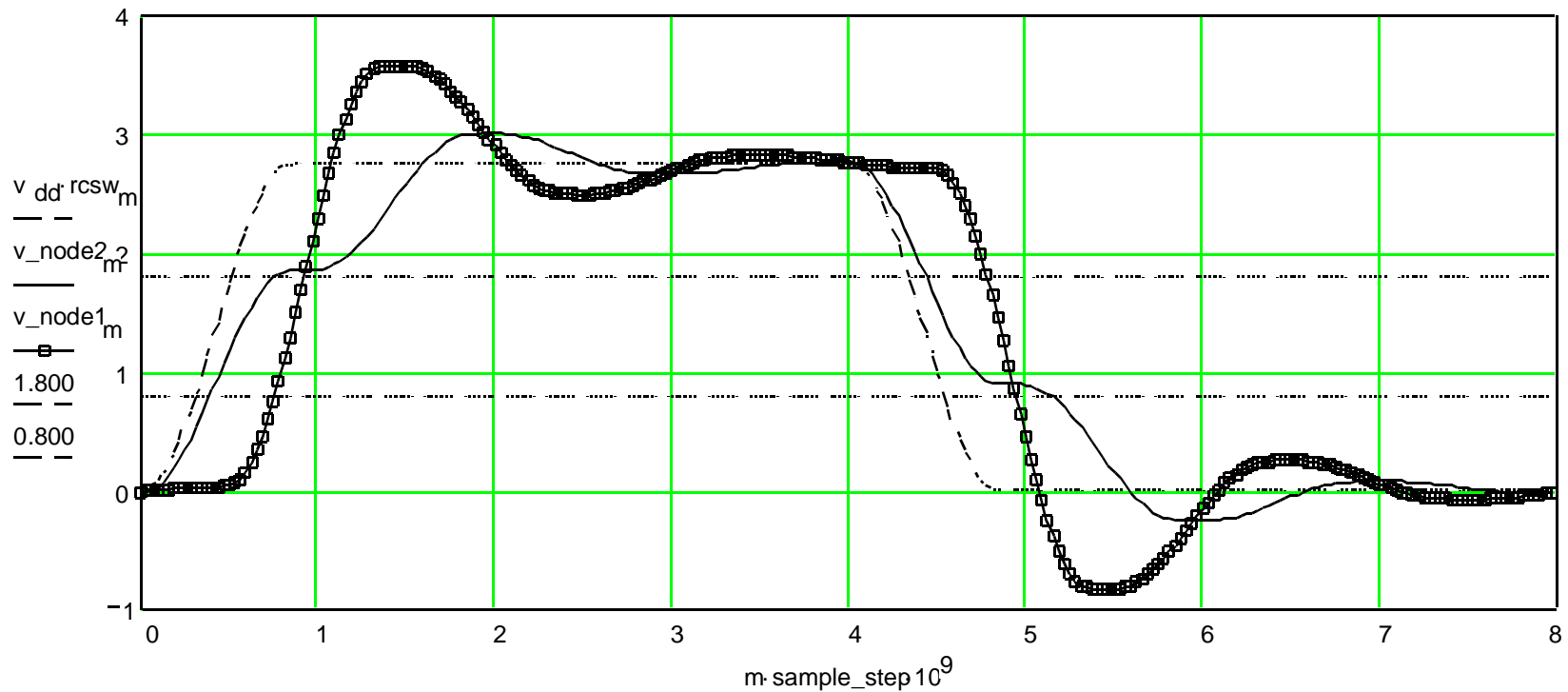

$v_{dd} = 2.75$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 3$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 25$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 0.5001$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$




## Overdrive: $R_{d\_out} = Z_o/2$

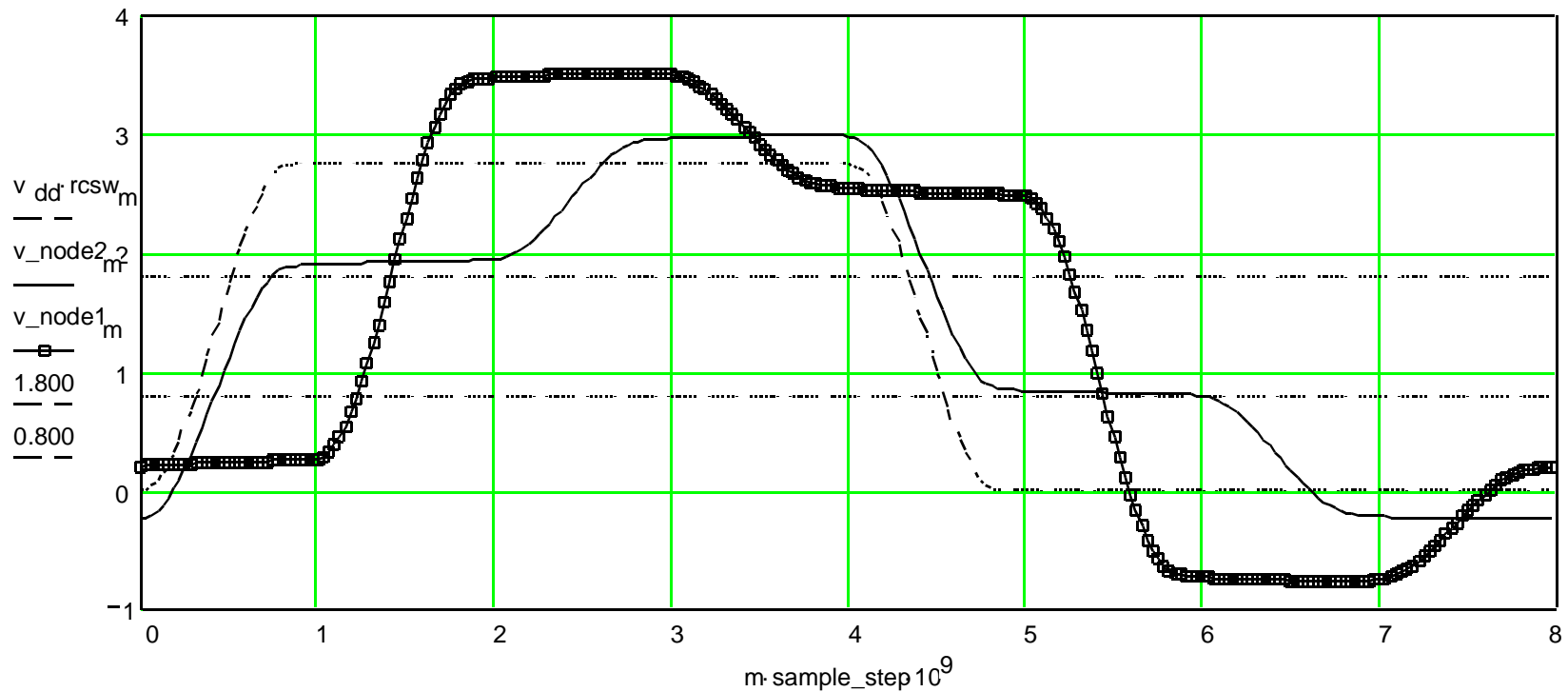

$v_{dd} = 2.75$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 25$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$


## Overdrive: $R_{d\_out} = Z_0/2$

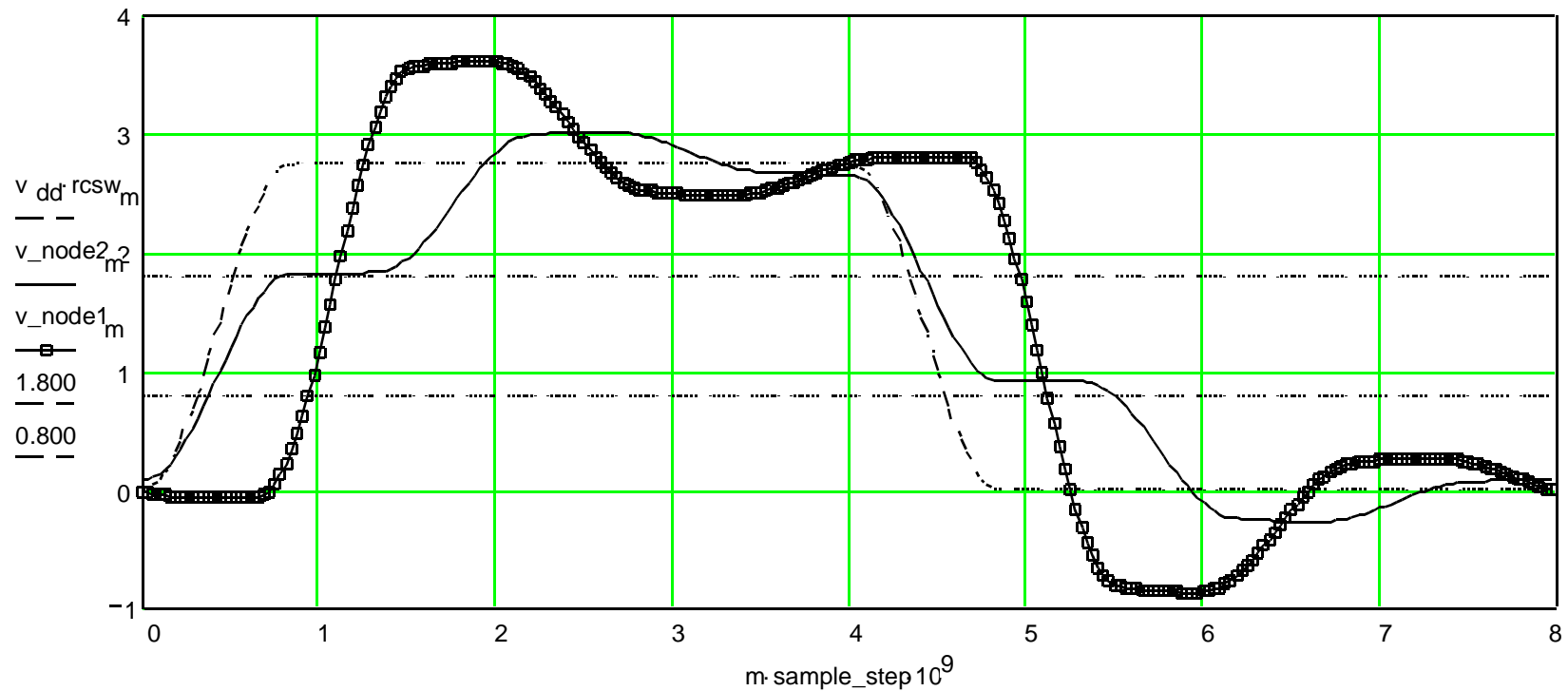

$v_{dd} = 2.75$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 4$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 25$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 0.6667$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$

**Ringings is greatest at 4 inches where the line has a weak resonance at 375 MHz**

## Overdrive: $R_{d\_out} = Z_o/2$

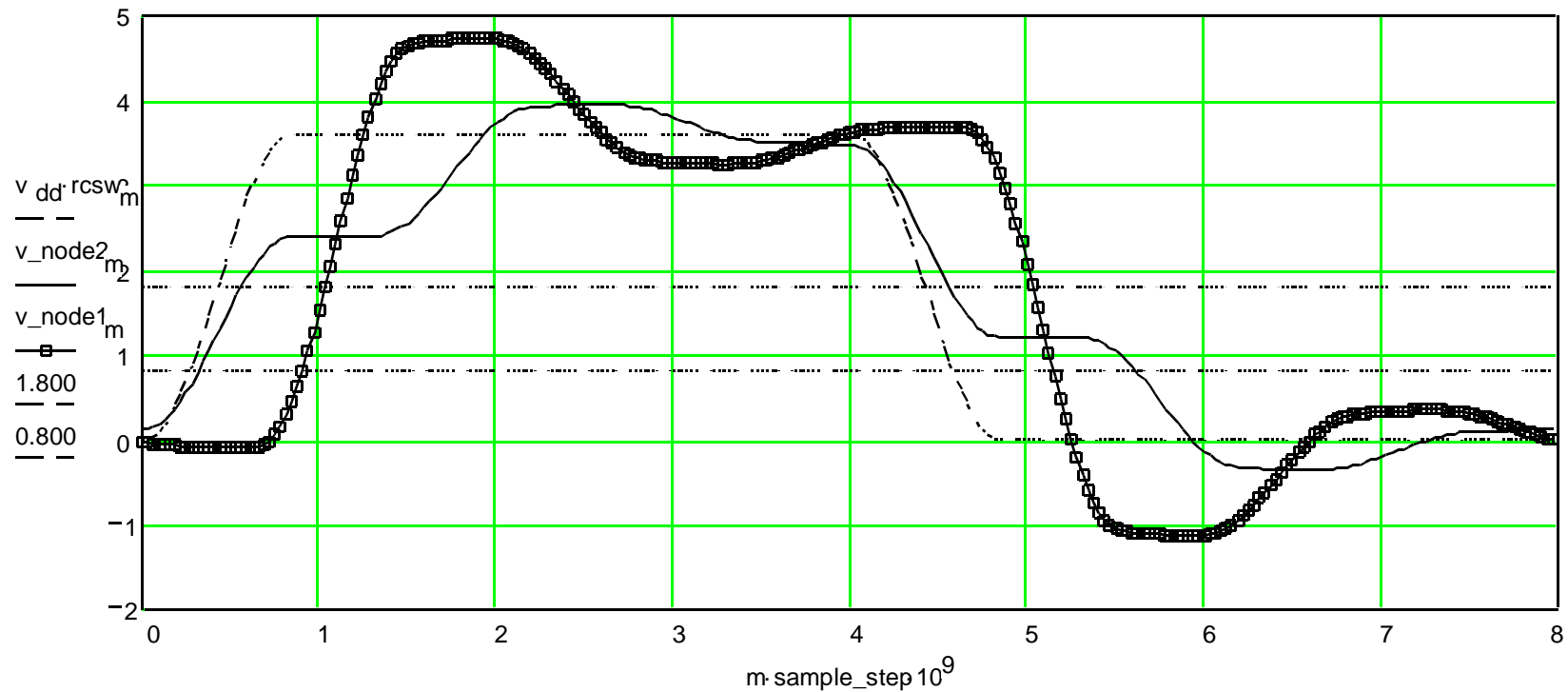

$v_{dd} = 3.6$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 0$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 4$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 25$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 0.6667$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$

**Overshoot is a problem for 3.3 Volt drivers, especially with 2.5 Volt receivers**


## What are the effects of the GMII receiver input parasitics on source and end terminated lines?

### Proposed values for input parasitics

Table 1:

Parameter	BGA	Lucent	National
Cr_pin	2.0 pF	4.0 pF	0.5 pF
Lr_sig_pin	6.0 nH	17.2 nH	10 nH
Lr_com_pin	2.0 nH	16.1 nH	10 nH
Cr_pad	2.0 pF	1.43 pF	4.5 pF


## Source (Series) Termination

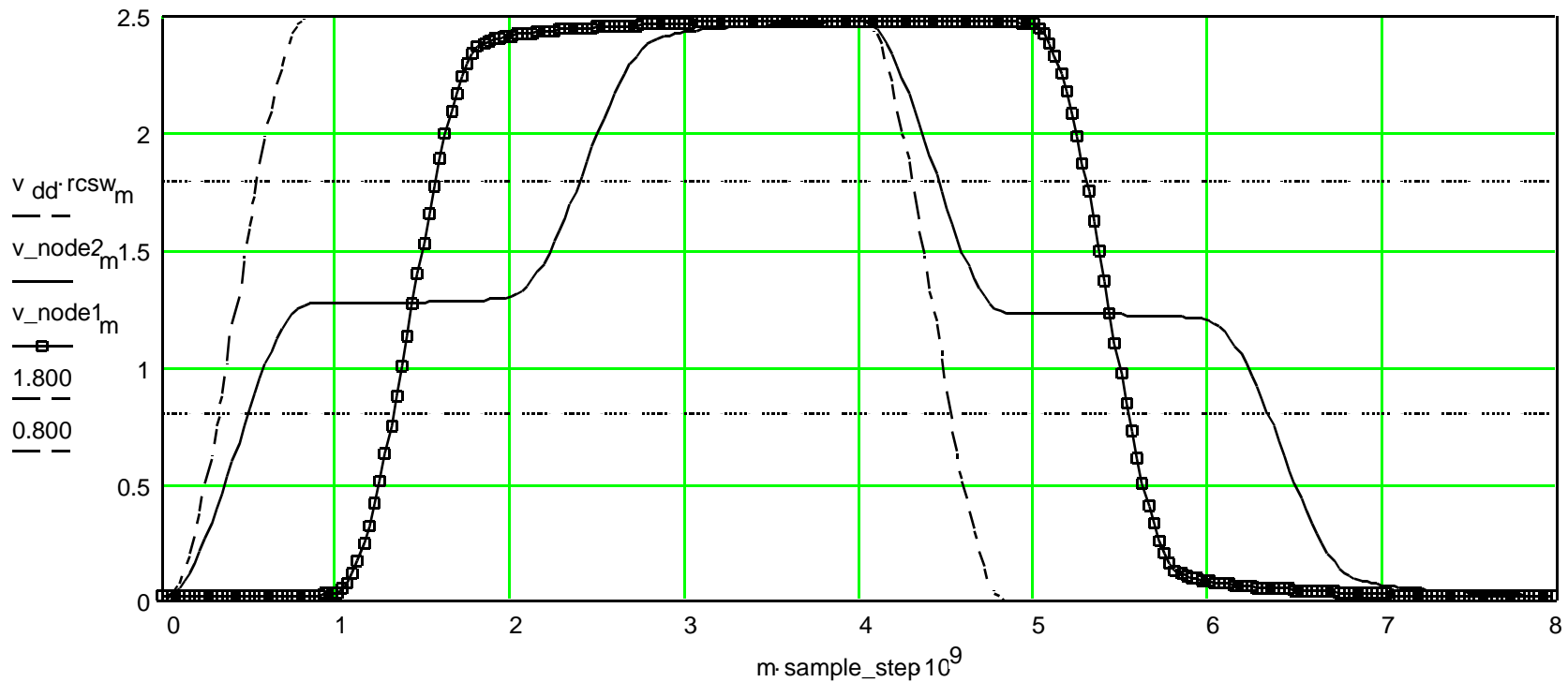

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 50$	$Z_o = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$

**No GMII receiver loading**


## Source (Series) Termination

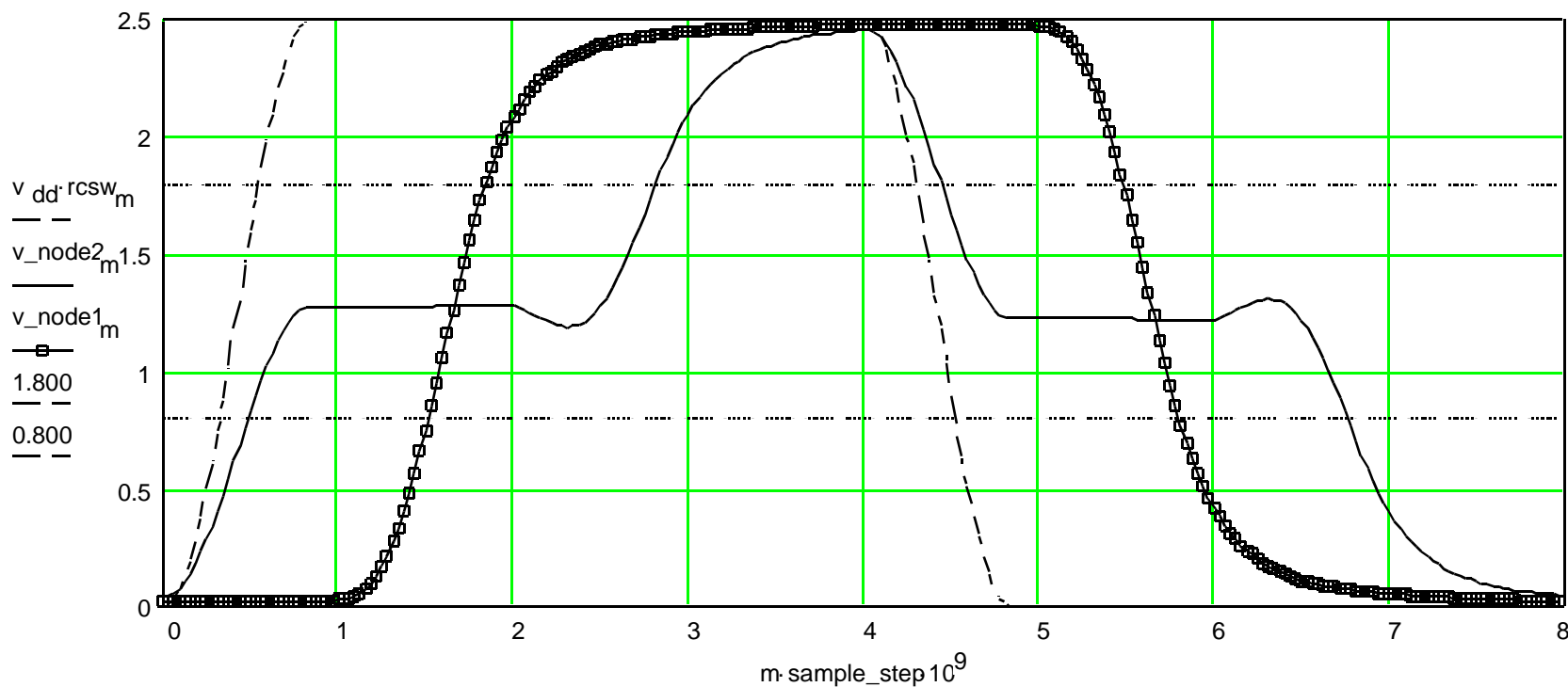

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 50$	$Z_o = 50$	$C_{r\_pin} = 2 \cdot 10^{-12}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 3 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-12}$

**5 pF at the GMII receiver end of the line**


## Source (Series) Termination

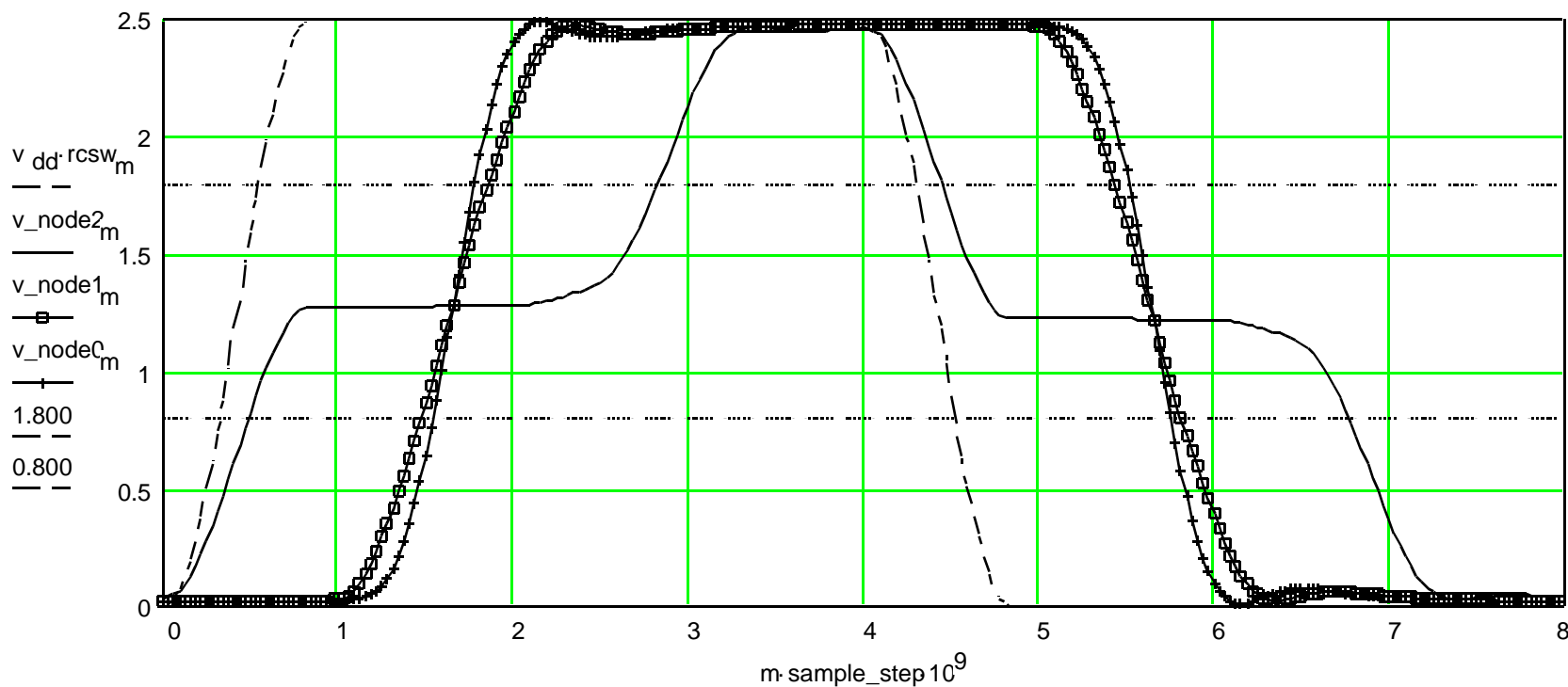

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 50$	$Z_o = 50$	$C_{r\_pin} = 2 \cdot 10^{-12}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 2 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_{r\_sig\_pin} = 6 \cdot 10^{-9}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 2 \cdot 10^{-9}$

**GMII receiver Pi network with BGA Values**

## Source (Series) Termination

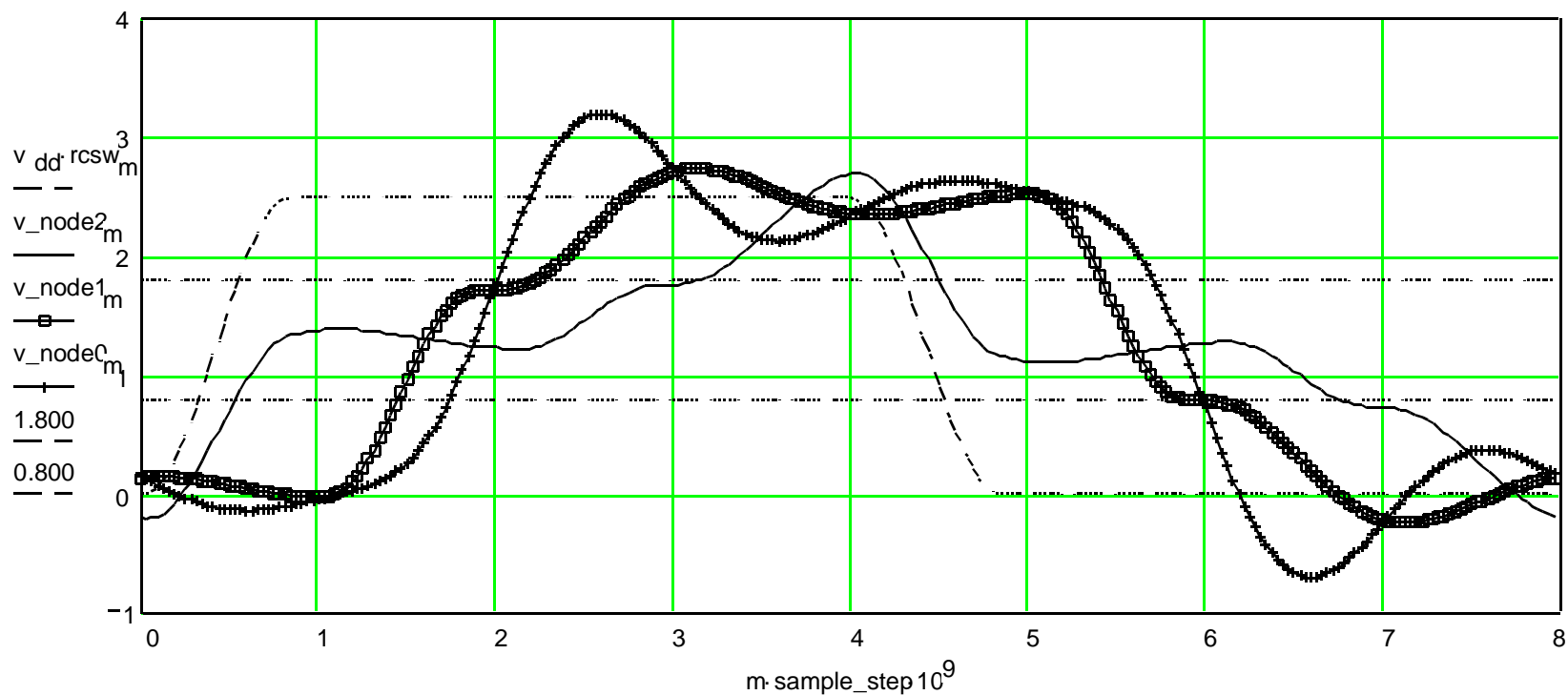


$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 50$	$Z_o = 50$	$C_{r\_pin} = 4 \cdot 10^{-12}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 1.43 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_{r\_sig\_pin} = 1.72 \cdot 10^{-8}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1.61 \cdot 10^{-8}$

### GMII receiver Pi network with Lucent Values




## Source (Series) Termination

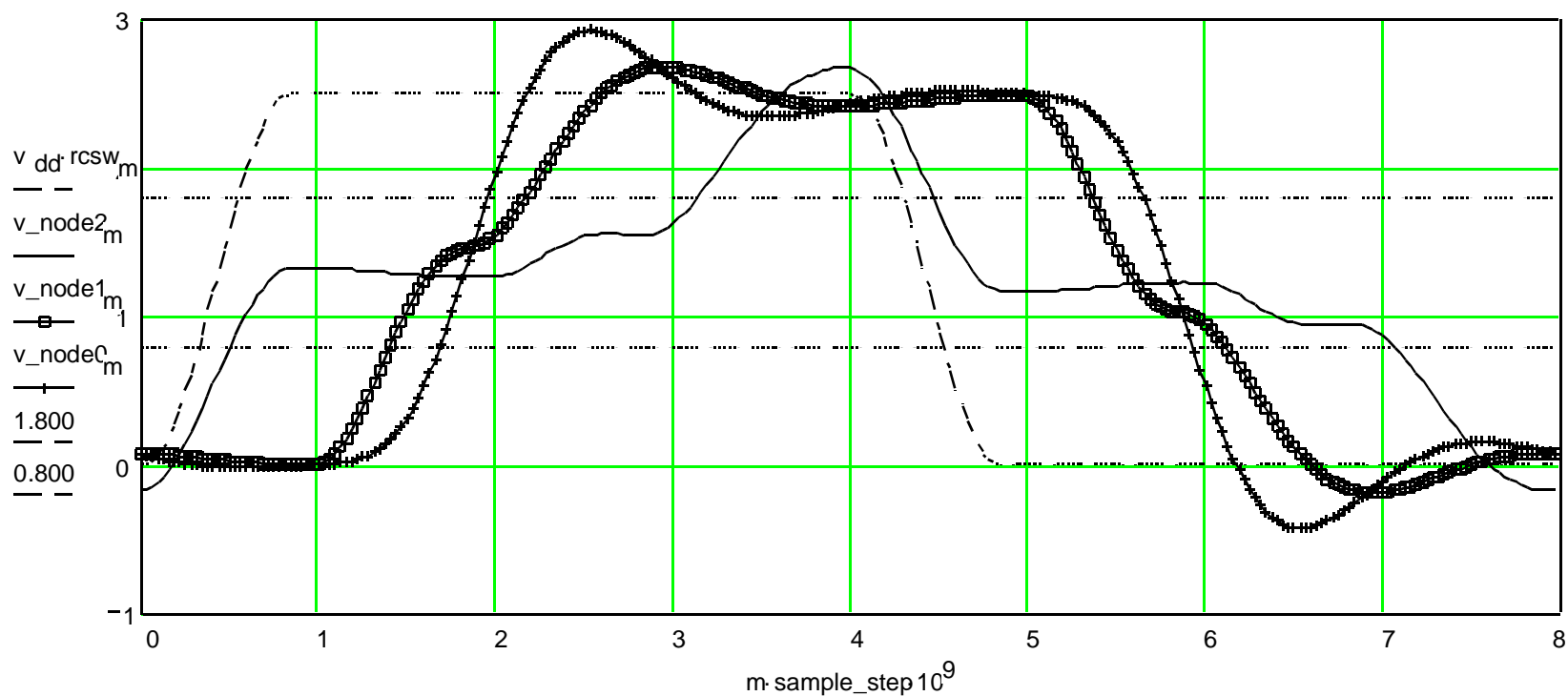

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 50$	$Z_o = 50$	$C_{r\_pin} = 5 \cdot 10^{-13}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 4.5 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_{r\_sig\_pin} = 1 \cdot 10^{-8}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1 \cdot 10^{-8}$

### GMI receiver Pi network with National Values


## Source (Series) Termination

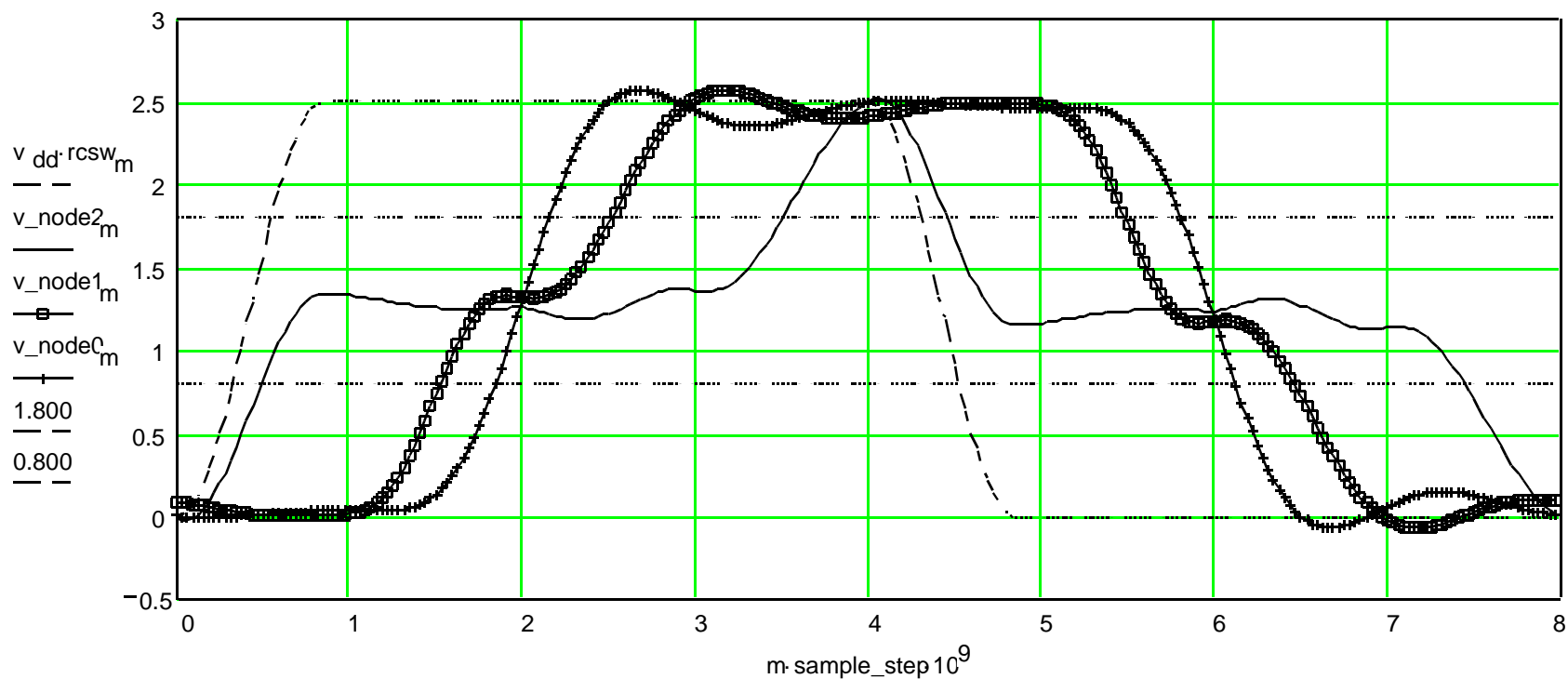

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$R_{ser} = 100$	$Z_o = 100$	$C_{r\_pin} = 4 \cdot 10^{-12}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$C_R = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_{r\_pad} = 1.43 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$L_R = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0002$	$L_{r\_sig\_pin} = 1.72 \cdot 10^{-8}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$			$L_{r\_com\_pin} = 1.61 \cdot 10^{-8}$

**GMII receiver Pi network with Lucent Values and 100 Ohm line**

## Source (Series) Termination

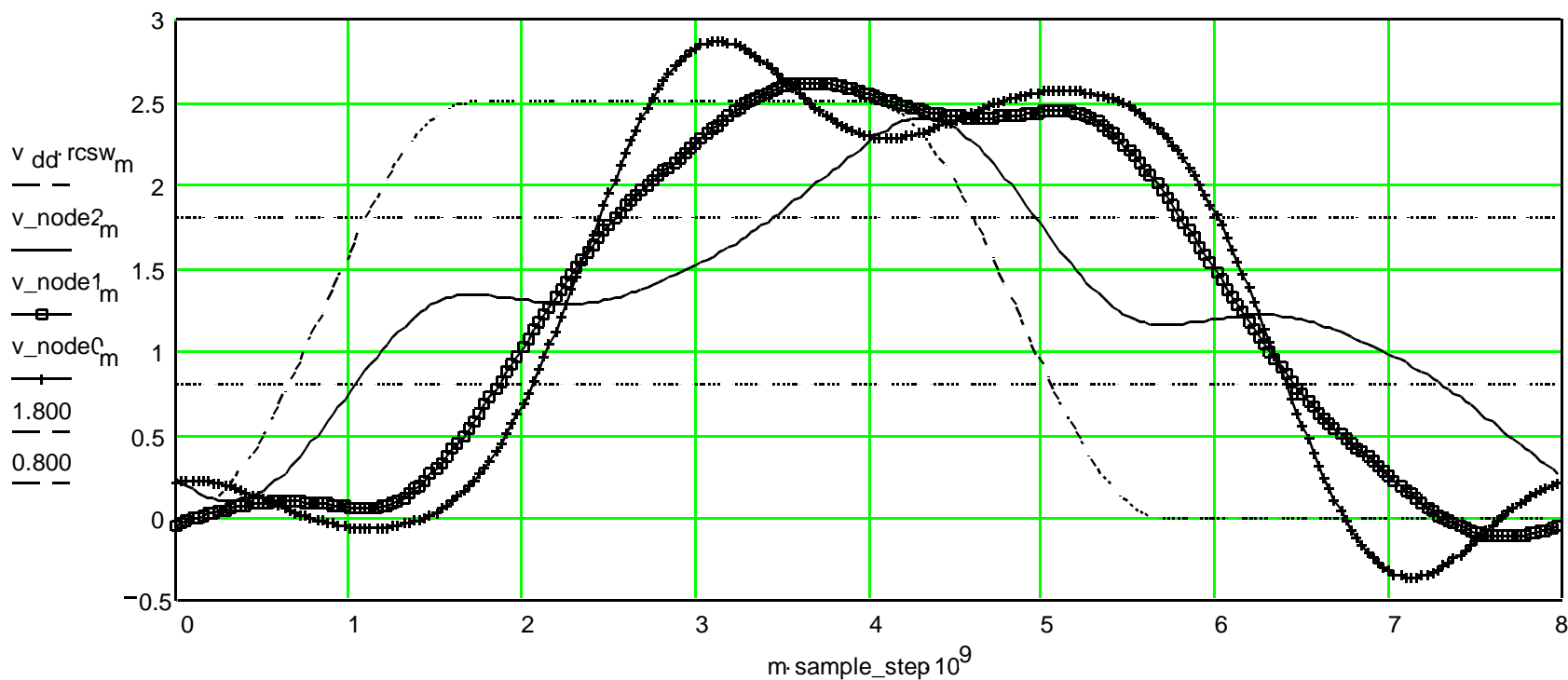

$$v_{dd} = 2.5$$

$$\text{rise\_time} = 1 \cdot 10^{-9}$$

$$R_{d\_out} = 0$$

$$C_{d\_pad} = 1 \cdot 10^{-15}$$

$$C_{d\_pin} = 1 \cdot 10^{-15}$$

$$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$$

$$L_{d\_com\_pin} = 1 \cdot 10^{-12}$$

$$R_{ser} = 50$$

$$C_R = 1 \cdot 10^{-15}$$

$$L_R = 1 \cdot 10^{-12}$$

$$Z_o = 50$$

$$\text{line\_length\_inch} = 6$$

$$\text{one\_way\_delay\_ns} = 1.0001$$

$$C_{r\_pin} = 4 \cdot 10^{-12}$$


$$C_{r\_pad} = 1.43 \cdot 10^{-12}$$

$$L_{r\_sig\_pin} = 1.72 \cdot 10^{-8}$$

$$L_{r\_com\_pin} = 1.61 \cdot 10^{-8}$$

**GMI receiver Pi network with Lucent Values and 1.0 ns risetime**


## End (Parallel) Termination

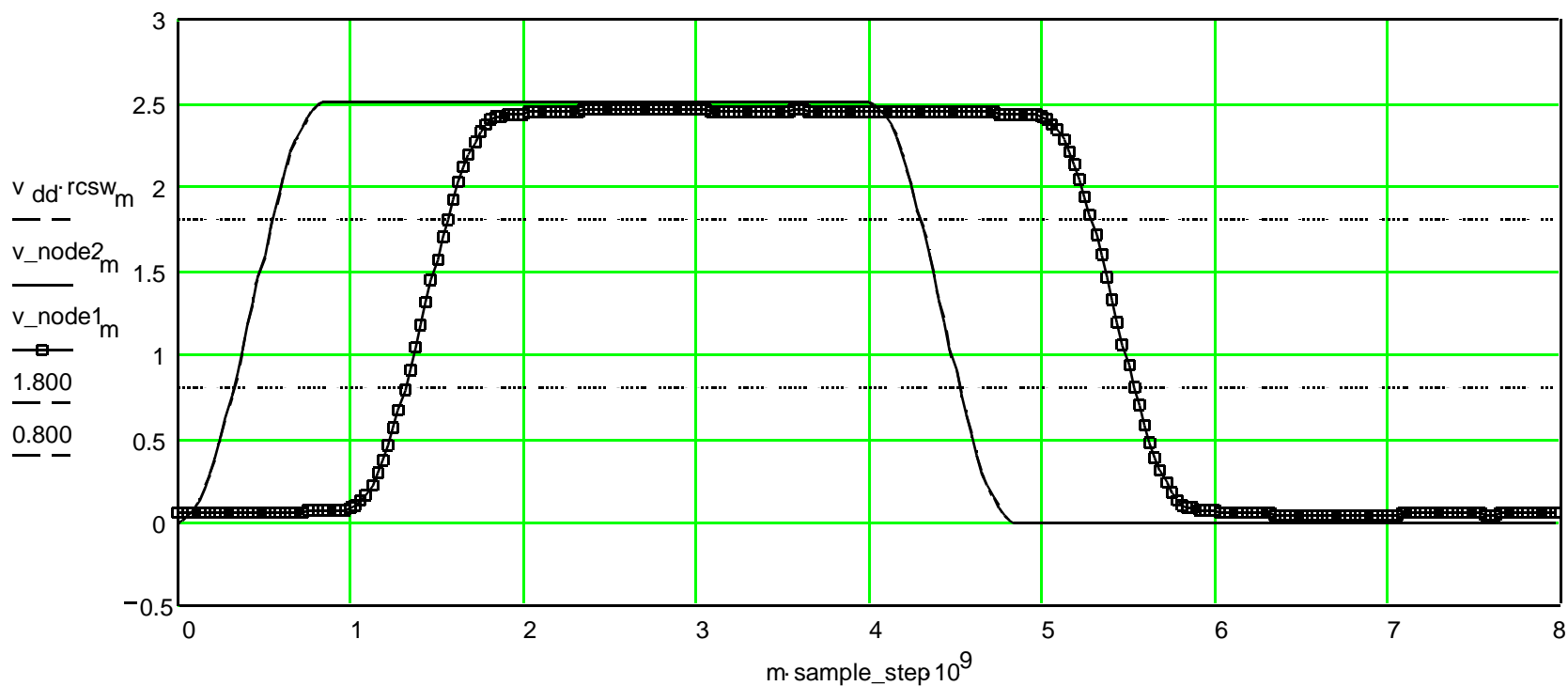

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$Z_o = 50$	$R_t = 50$	$C_{r\_pin} = 1 \cdot 10^{-15}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_R = 1 \cdot 10^{-15}$	$C_{r\_pad} = 1 \cdot 10^{-15}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_R = 1 \cdot 10^{-12}$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$		$v_t = 1.25$	$L_{r\_com\_pin} = 1 \cdot 10^{-12}$

**No GMII receiver loading**


## End (Parallel) Termination

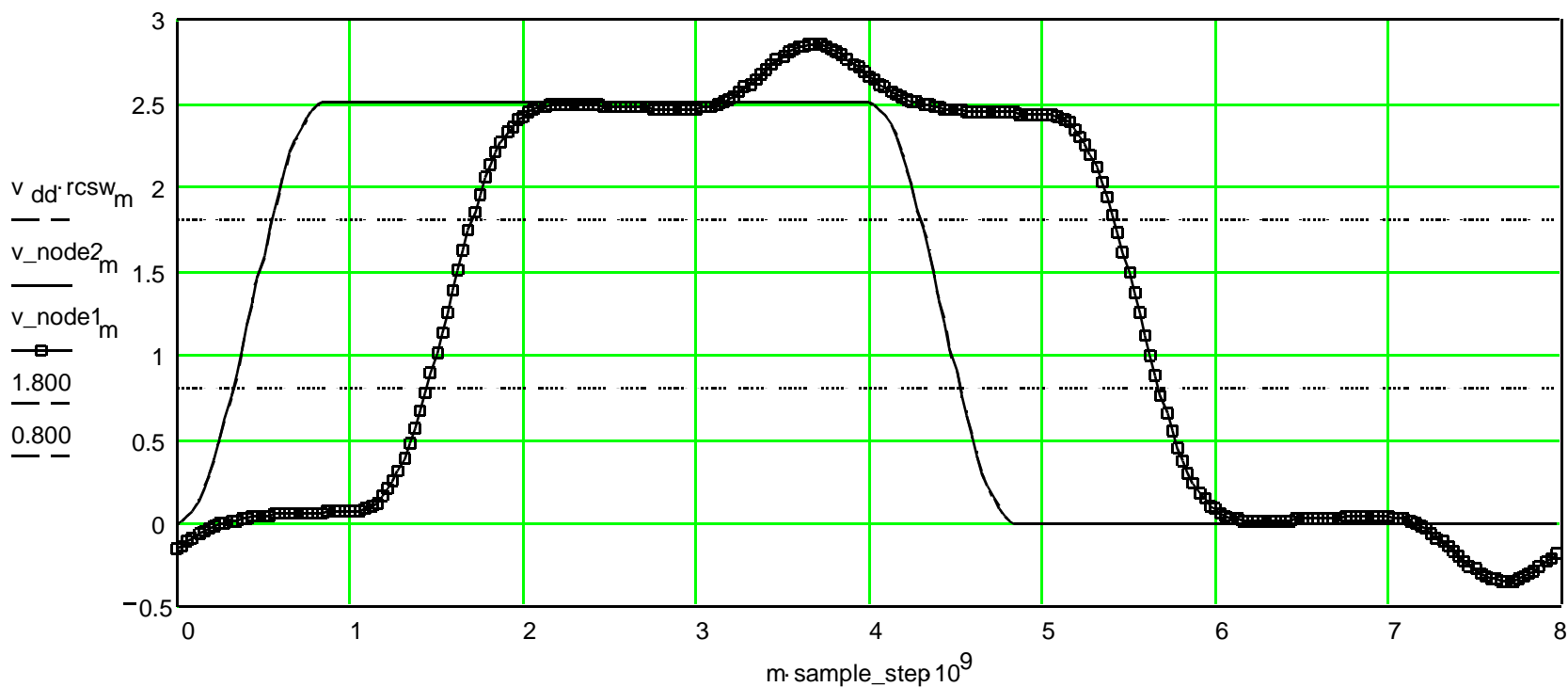

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$Z_o = 50$	$R_t = 50$	$C_{r\_pin} = 2 \cdot 10^{-12}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_R = 1 \cdot 10^{-15}$	$C_{r\_pad} = 3 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_R = 1 \cdot 10^{-12}$	$L_{r\_sig\_pin} = 1 \cdot 10^{-12}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$		$v_t = 1.25$	$L_{r\_com\_pin} = 1 \cdot 10^{-12}$

**5 pF at the GMII receiver end of the line**


## End (Parallel) Termination

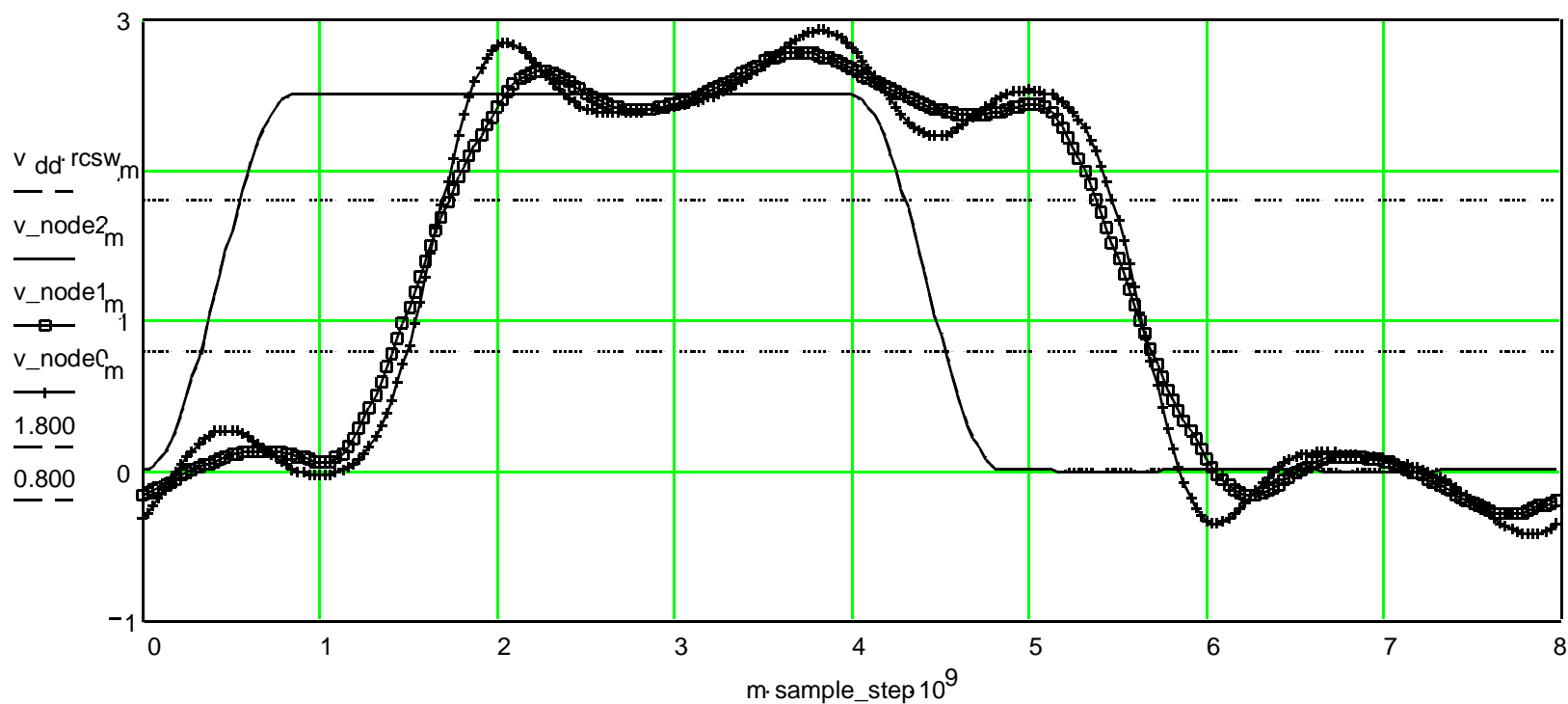

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$Z_o = 50$	$R_t = 50$	$C_{r\_pin} = 2 \cdot 10^{-12}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_R = 1 \cdot 10^{-15}$	$C_{r\_pad} = 2 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_R = 1 \cdot 10^{-12}$	$L_{r\_sig\_pin} = 6 \cdot 10^{-9}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$		$v_t = 1.25$	$L_{r\_com\_pin} = 2 \cdot 10^{-9}$

### GMII receiver Pi network with BGA Values


## End (Parallel) Termination

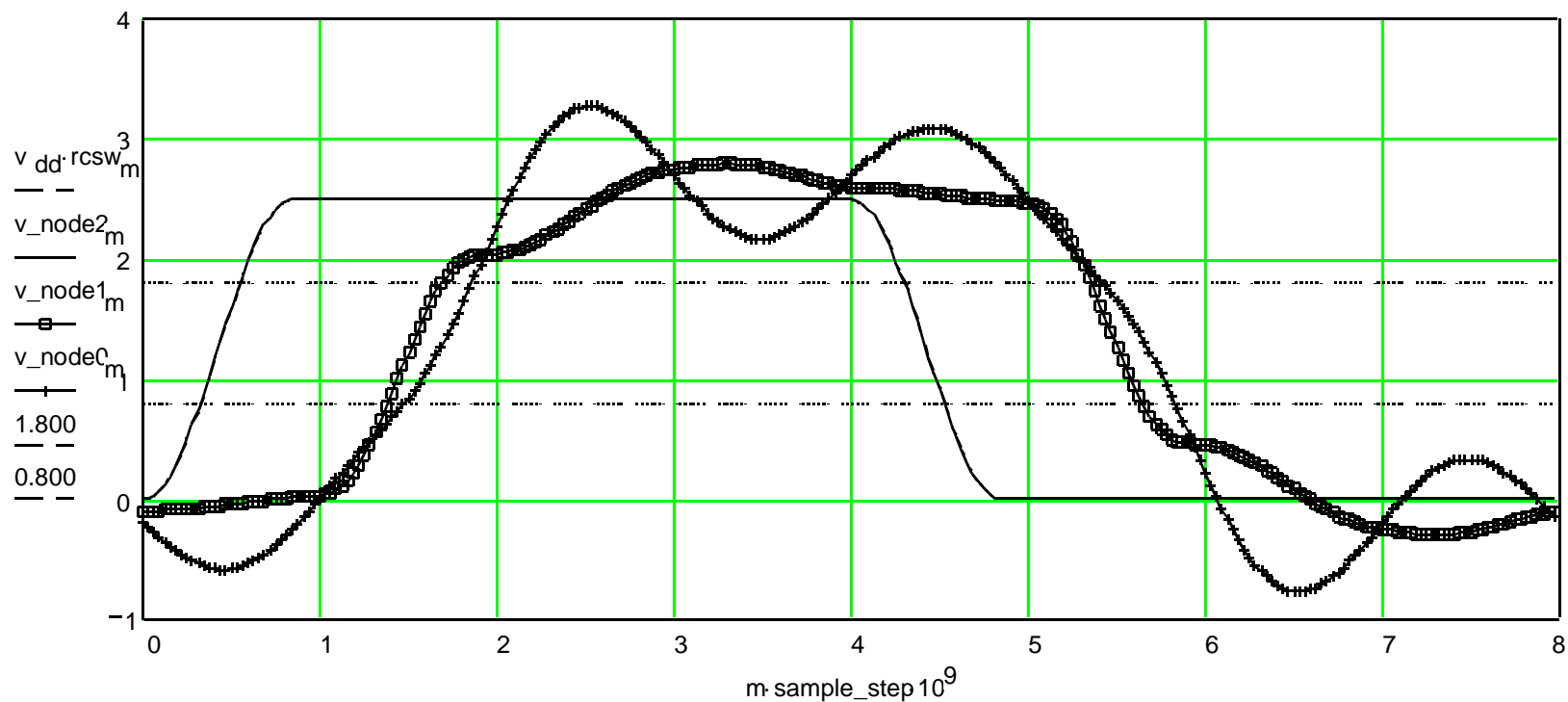

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$Z_o = 50$	$R_t = 50$	$C_{r\_pin} = 4 \cdot 10^{-12}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_R = 1 \cdot 10^{-15}$	$C_{r\_pad} = 1.43 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_R = 1 \cdot 10^{-12}$	$L_{r\_sig\_pin} = 1.72 \cdot 10^{-8}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$		$v_t = 1.25$	$L_{r\_com\_pin} = 1.61 \cdot 10^{-8}$

### GMII receiver Pi network with Lucent Values

## End (Parallel) Termination

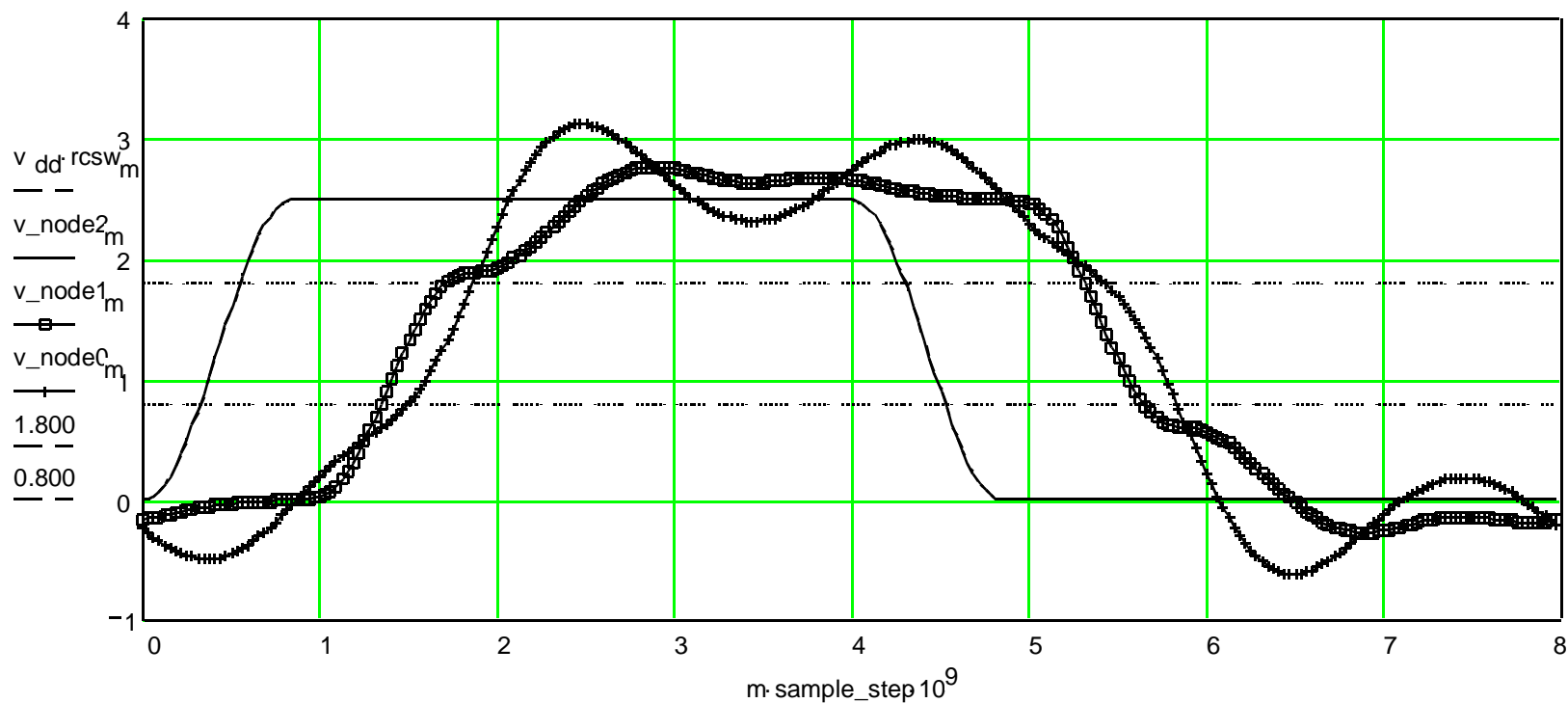


$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$Z_o = 50$	$R_t = 50$	$C_{r\_pin} = 5 \cdot 10^{-13}$
$rise\_time = 5 \cdot 10^{-10}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_R = 1 \cdot 10^{-15}$	$C_{r\_pad} = 4.5 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_R = 1 \cdot 10^{-12}$	$L_{r\_sig\_pin} = 1 \cdot 10^{-8}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$		$v_t = 1.25$	$L_{r\_com\_pin} = 1 \cdot 10^{-8}$

**GMI receiver Pi network with National Values**



## End (Parallel) Termination

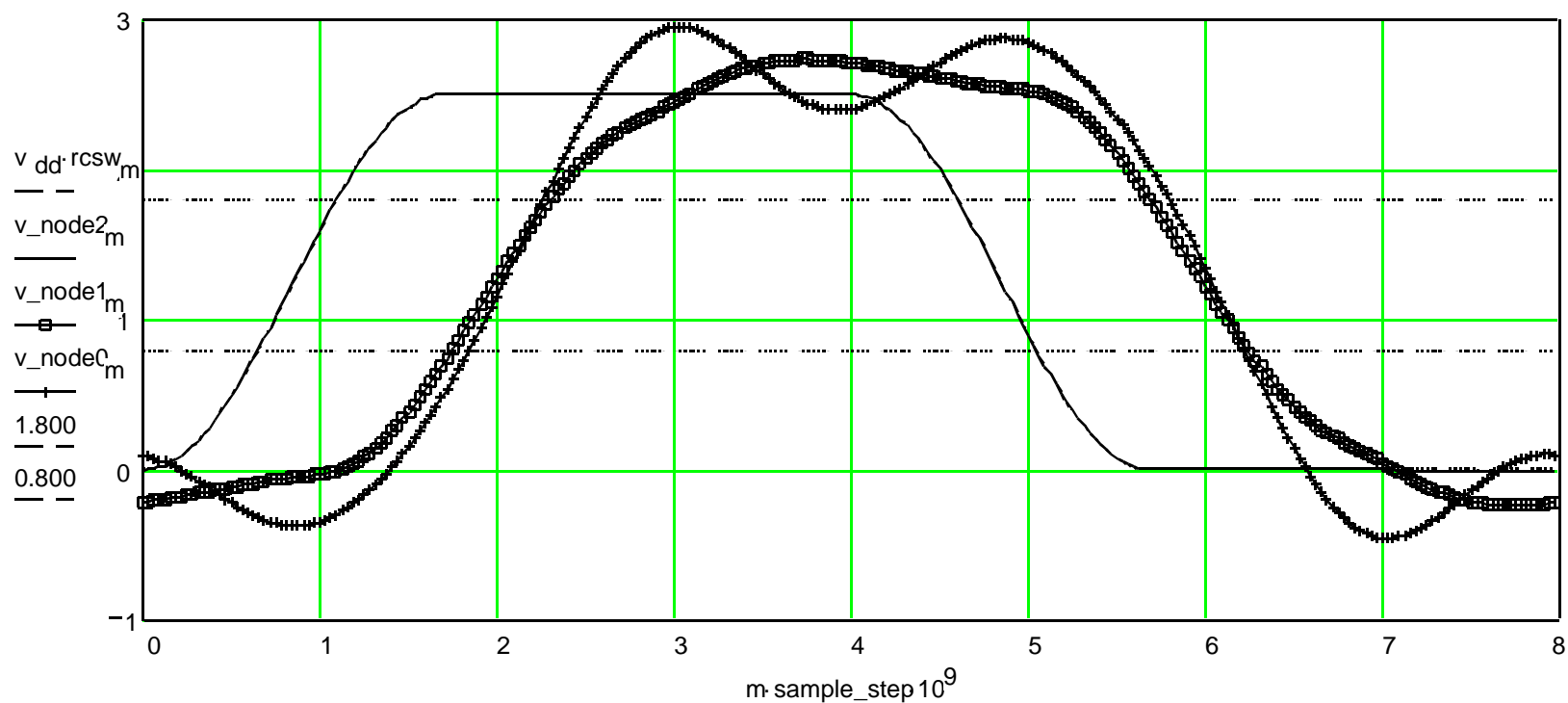

$v_{dd} = 2.5$	$C_{d\_pad} = 1 \cdot 10^{-15}$	$Z_o = 50$	$R_t = 50$	$C_{r\_pin} = 4 \cdot 10^{-12}$
$rise\_time = 1 \cdot 10^{-9}$	$C_{d\_pin} = 1 \cdot 10^{-15}$	$line\_length\_inch = 6$	$C_R = 1 \cdot 10^{-15}$	$C_{r\_pad} = 1.43 \cdot 10^{-12}$
$R_{d\_out} = 0$	$L_{d\_sig\_pin} = 1 \cdot 10^{-12}$	$one\_way\_delay\_ns = 1.0001$	$L_R = 1 \cdot 10^{-12}$	$L_{r\_sig\_pin} = 1.72 \cdot 10^{-8}$
	$L_{d\_com\_pin} = 1 \cdot 10^{-12}$		$v_t = 1.25$	$L_{r\_com\_pin} = 1.61 \cdot 10^{-8}$

**GMII receiver Pi network with Lucent Values and 1.0 ns risetime**

# Proposed GMII Electrical Specifications

## DC Specifications

The DC characteristics of GMII drivers and receivers shall comply with the values given in the following table.

Symbol	Parameter	Conditions		Min	Max	Units
V <sub>OH</sub>	Output High Voltage	I <sub>OH</sub> = -1.0mA	V <sub>CC</sub> = Min	2.00	V <sub>CC</sub>	V
V <sub>OL</sub>	Output Low Voltage	I <sub>OL</sub> = 1.0mA	V <sub>CC</sub> = Min	GND	0.40	V
V <sub>IH</sub>	Input High Voltage			1,60	-	V
V <sub>IL</sub>	Input Low Voltage			-	0,80	V
I <sub>IH</sub>	Input High Current	V <sub>CC</sub> = Max	V <sub>IN</sub> = 2.0V	-	40	μA
I <sub>IL</sub>	Input Low Current	V <sub>CC</sub> = Max	V <sub>IN</sub> = 0.4V	-600	-	μA


<sup>1</sup> V<sub>CC</sub> equal to 3.6V max.

## AC Specifications

The minimum setup time and hold time of a GMII receiver shall be 2.0 ns and 1.0 ns respectively.

The input signal at the pins of a GMII receiver shall comply with the “GMII Receiver Input Potential Template” shown in the following figure.
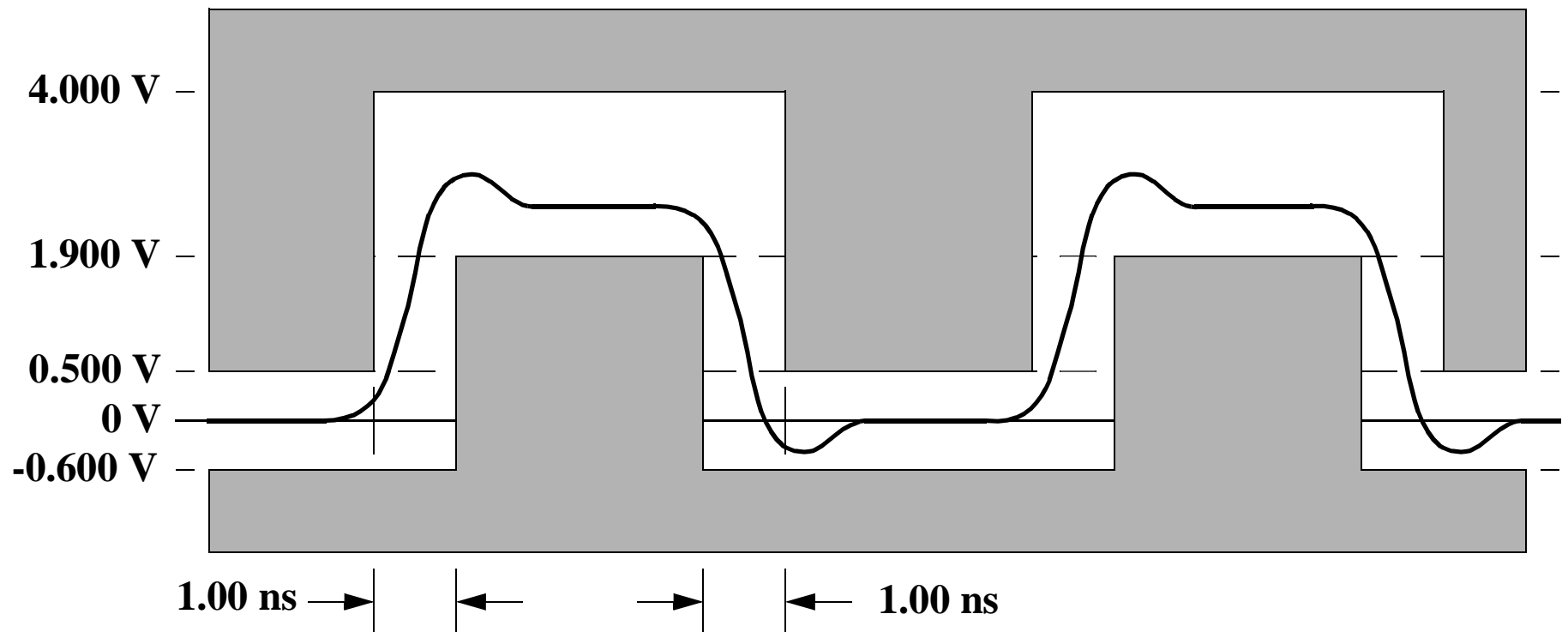
### GMII Receiver Input Potential Template



The signal at the receiver end of the 1.00 ns delay, 50 Ohm +/- 15% transmission line shown in the following figure shall comply with the "GMII Receiver Input Potential Template" when the transmission line is driven by a GMII driver and terminated with the termination network specified the vendor of the driver for this application.

