

# Vport static and transient response

**Fred Schindler**  
**Cisco Systems**


## Contributions by:

Taugfigue Ahmed	Akros Silicon	Chad Jones	Cisco Systems
Brian Buckmeir	Bel	Matthew Landry	Silicon Labs
Yair Darshan	PowerDsine	David Law	3COM
Bill Delveaux	Cisco Systems	Raul Lozano	Pulse
Wael Diab	Broadcom	Thong Nguyen	Maxim
Thuyen Dinh	Pulse	Ramesh Sastry	Cisco Systems
Sajol Ghoshal	Akros Silicon	Fred Schindler	Cisco Systems
Keith Hopwood	Phihong	Clay Stanford	Linear Technology

# Agenda

- Estimate the minimum static MDI voltage.
- Cover the team's next step.


# Typical PSE

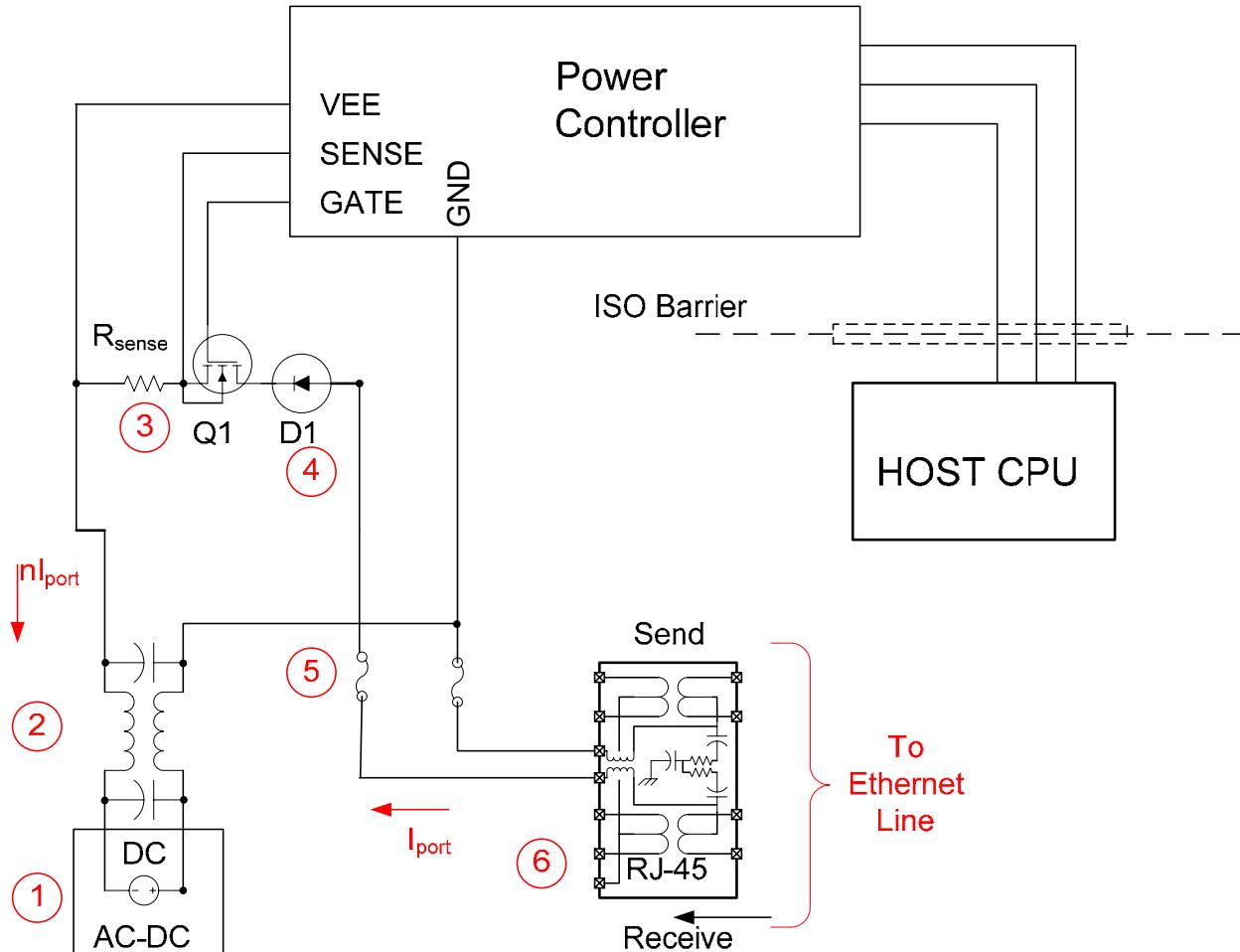

One port of a multiport PSE providing power on 2-cable pairs.

# Major Voltage Drop Sources

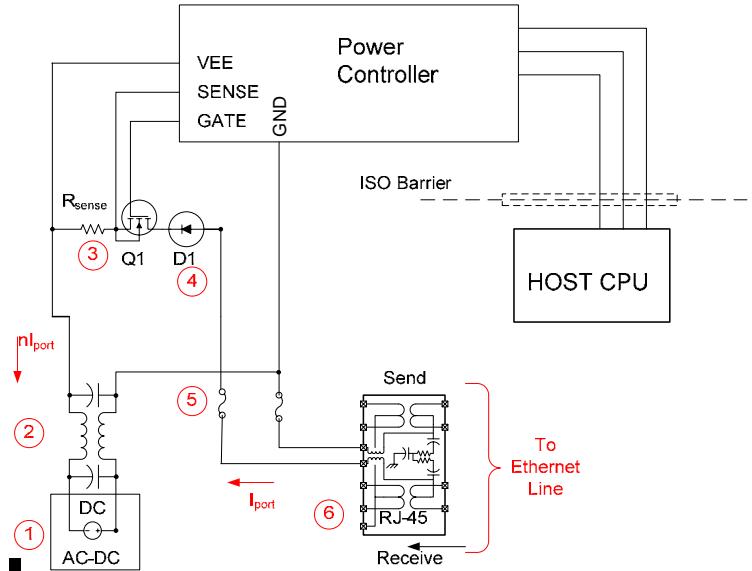- 1) AC-DC Power Supply**
  - Tolerance
  - Load
  - Transient response
- 2) CM Choke & PCB**
- 3) Rsense & MOSFET**
  - Value, internal/external
- 4) Pass diode**
  - Presence & type
- 5) Fuses**
  - Presence & type
- 6) PHY Transformer**



# Considerations

- Multiple system designs use the same power supply.
- Systems have different:
  - Circuit topology
  - Circuit elements
  - PoE modules
- Systems need to work under all loading conditions:
  - < 0.5 W to PoEplus per port
  - 1 to n ports

# Main Parameters


- AC-DC
  - ±3.7% tolerance**
  - 50 mohm output resistance**
  - CM choke + PCB, 30 mohm**
- Port
  - Rsense + MOSFET 0.53 to 1.5-ohm**
  - Diode 0 to 0.7-V**
  - Fuse 0 to 2x0.5-ohm**
  - Transformer and choke 0.5 ohm**
  - 48 ports**
- Cable
  - CAT-5**

# Why 48 ports?


- Focus on broadest part of the market.  
 $15.4 \text{ W} \times 48 = 740 \text{ W}$  for PoE  
Lower power levels fit within this constraint.
- 15 A, AC power circuit in Japan (100 VAC)  
700 W of PoE power available  
200 W of nonPoE power available  
75% breaker derate, 80% AC-DC efficiency
- Higher port count systems need to be optimized to fit within the calculated values.
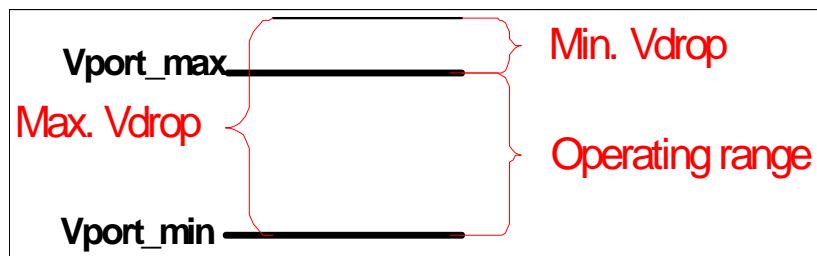
# Method

- Calculate the maximum and minimum drops from the power supply to the MDI.
- Maximum drop:
  - Maximum PoE power draw.
  - Largest path resistance and voltage drops.
- Minimum drop:
  - One port on at minimum holding current.
  - Lowest path resistance and voltage drops.
- Optimize results for the always-present minimum voltage drop.




# Minimum Static PSE Port Voltage

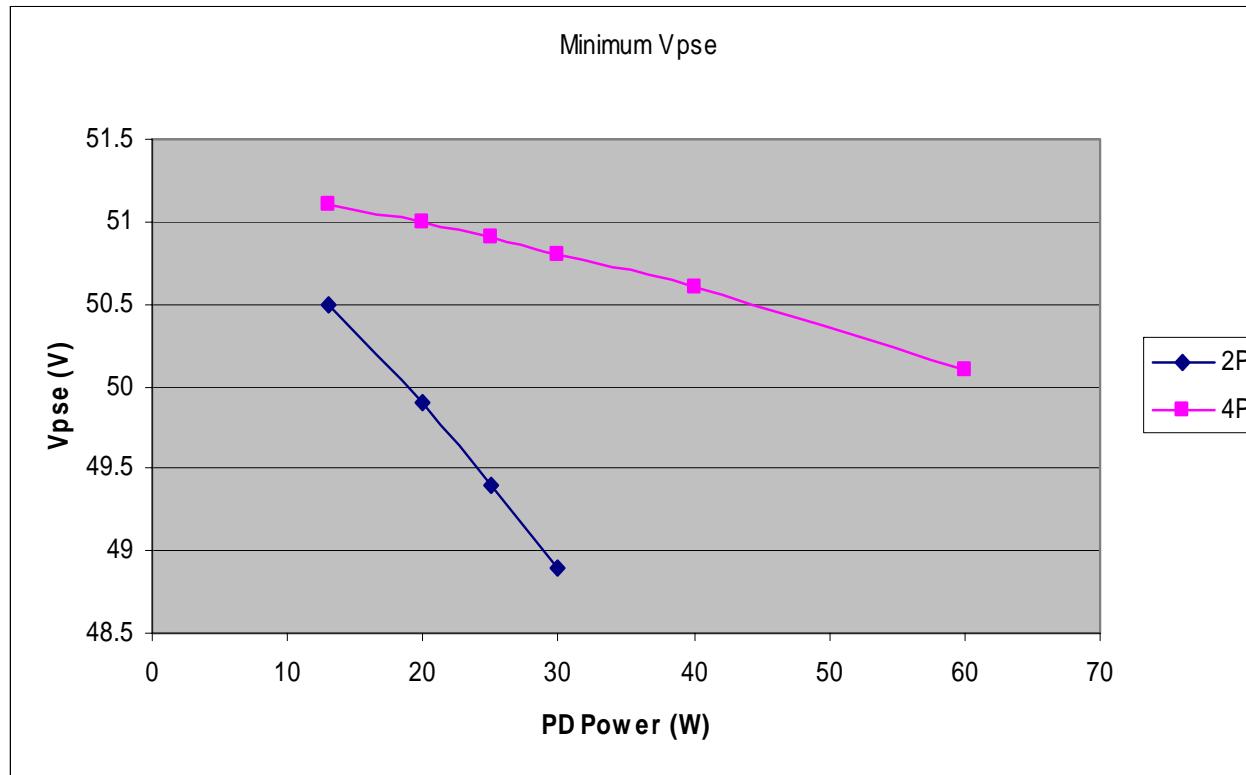


**2-pair 48.9 V, 4-pair 50.1 V**

# Minimum Static PD Port Voltage

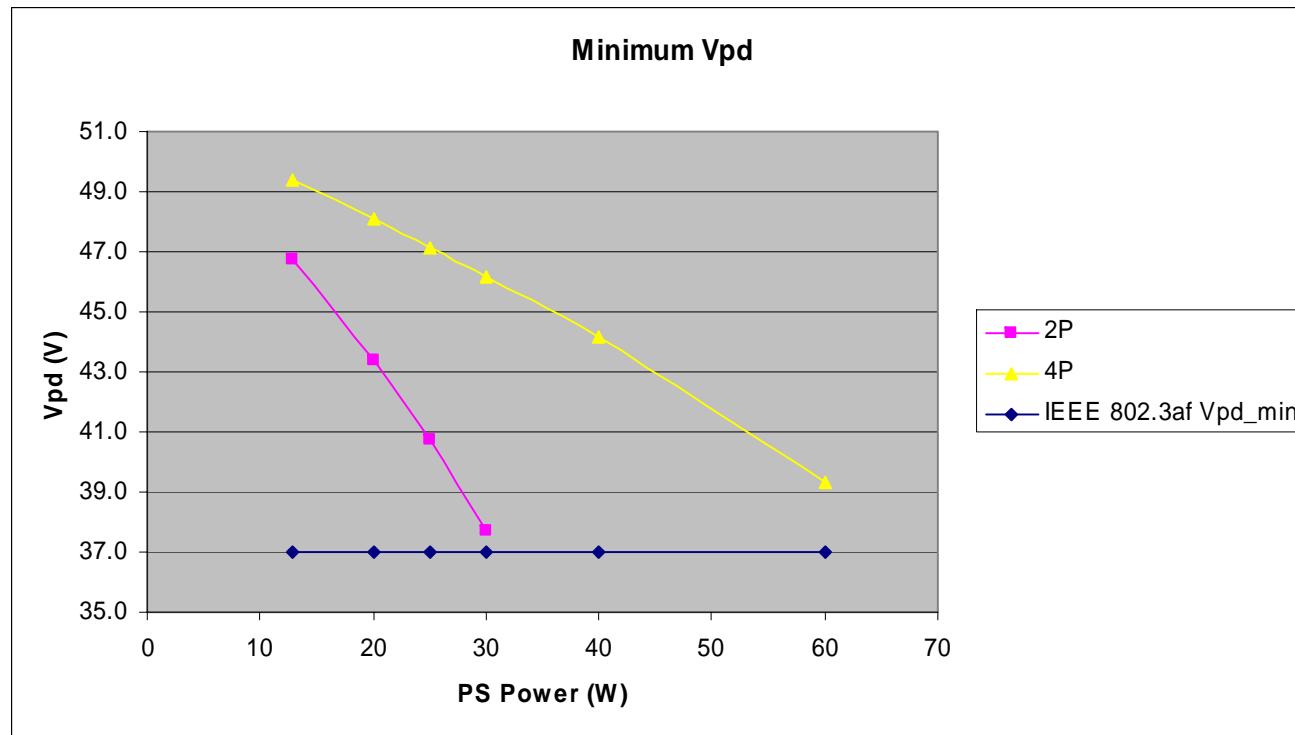

**2-pair 37.7 V, 4-pair 39.3 V**

# Nominal Wire current

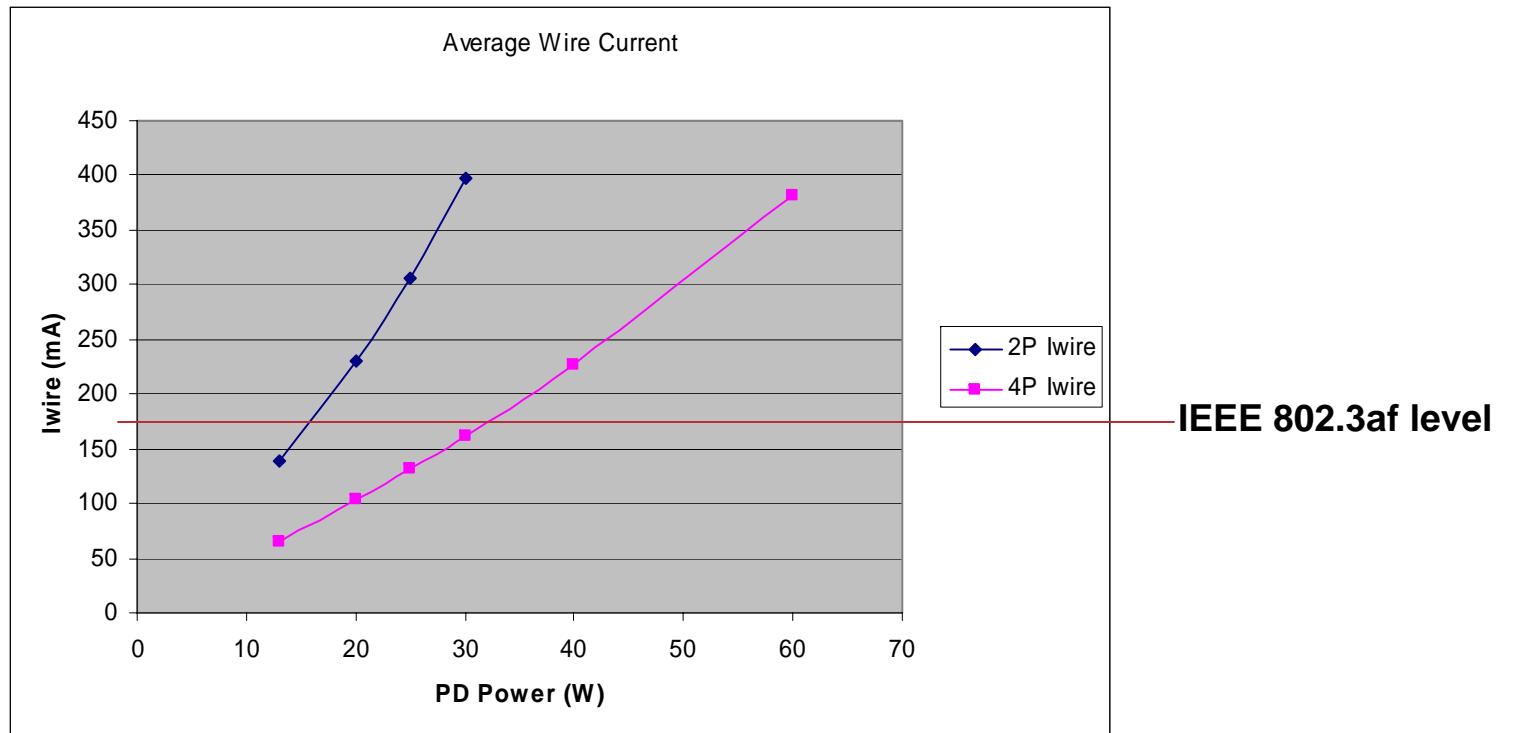

# Can the minimum port voltage be increased?

- A change in MDI voltage leads to a similar change in MDI current.
- Three things that reduce the MDI current (2 pair shown):
  - Move to DC-disconnect (0.7V → 0V)**  
Iwire 398→390mA, Vport\_min 48.9→49.4V
  - Improve AC-DC tolerance ( $\pm 3.7\%$ → $\pm 1.5\%$ )**  
Iwire 390→357mA, Vport\_min 49.4→52.1V
  - Use a wire fuse and better MOSFET (2.5→1.5ohm)**  
Iwire 357→350mA, Vport\_min 52.1→52.8V
- A minimum port voltage in the range of 49 to 53-V is achievable but increasing the voltage above 49 V can reduce suppliers-supporting the IEEE 802.3at specification.

# Recommendations for Static Port Voltage

- The PD minimum port voltage ensures compatibility with IEEE 802.3af.
- The 30 W 2 pair IEEE 802.3at requirement has been met.
- The PSE minimum port voltage is raised from 44 V to 50 V.

PD circuit margin is 2.2 V.

PD circuit margin for IEEE 802.3af was 1.0 V.

At a PSE port voltage of 48.5 V, the PD margin is the same as it is for IEEE 802.3af.

At a PSE port voltage of 44.0 V, the wire current increases 25% for a 2-pair system, and the PD voltage would drop to 29.8 V (30 W @ PD).

# Agenda

- Estimate the minimum static MDI voltage.
- Cover the team's next step.

# Dynamic Port Voltage

- **Goal: Specify the dynamic port voltage. Provide bounds that designs can meet.**
- **Identify existing constraints.**

**Load change**

**$di/dt \leq 35 \text{ mA/uS}$  (This may be a condition for a requirement.)**

**$dV/dt \leq 3.5 \text{ V/uS}$ .**

**$I_{CUT}$**

**$I_{LIM}$**

- **Dealing with backing up the system power supply.**
- **Review system solutions for dealing with transients.**

# **Questions ...**

**... or comments**