

Project: IEEE P802.15 Working Group for Wireless Personal Area Networks (WPANs)

Submission Title: Current Status of Semiconductor Technologies and Circuits for THz applications

Date Submitted: July 2008

Source: Jae-Sung Rieh, Korea University

Address

Voice: FAX: E-Mail: jsrieh@korea.ac.kr

Re:

Abstract: Current Status of Semiconductor Technologies and Circuits for THz applications

Purpose:

Notice: This document has been prepared to assist the IEEE P802.15. It is offered as a basis for discussion and is not binding on the contributing individual(s) or organization(s). The material in this document is subject to change in form and content after further study. The contributor(s) reserve(s) the right to add, amend or withdraw material contained herein.

Release: The contributor acknowledges and accepts that this contribution becomes the property of IEEE and may be made publicly available by P802.15.

Current Status of Semiconductor Technologies and Circuits for THz applications

2008. 7.16

Jae-Sung Rieh
School of Electrical Engineering
Korea University


Outline

- Introduction
- Components for THz Communication Systems
- Semiconductor Technologies for THz
- Circuit Examples for THz
- Summary

Introduction

- Two main approaches for THz system implementation
 - Optical approach
 - Challenge: lowering the operation frequency
 - Electrical approach
 - Challenge: raising the operation frequency
- Electrical approaches
 - Diode approach
 - Passive and no gain provided
 - Transistor approach
 - Operation frequency still not sufficient but growing


Traditional Diode-Based THz Receiver

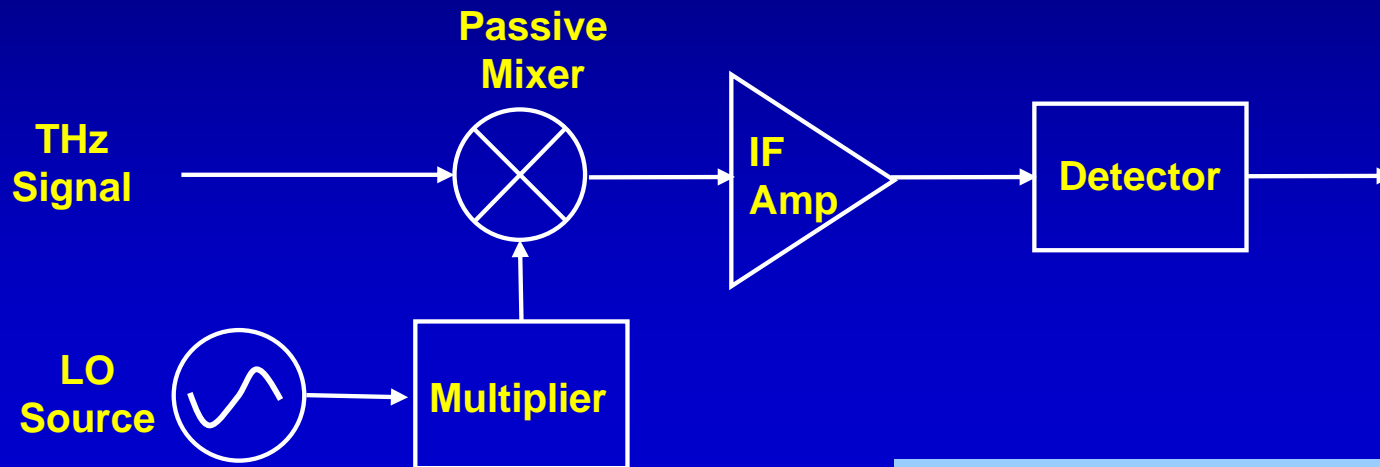

$$F = F_{mixer} + L_{Mixer} (F_{IFamp} - 1) + \dots$$

- Issues
 - Absence of LNA
 - Noise from mixer and IF amp not suppressed
 - Passive nature of mixer
 - No gain provided. Noise from IF amp not suppressed
 - LO source
 - Typically not integration-ready

Transistor-Based THz Receiver

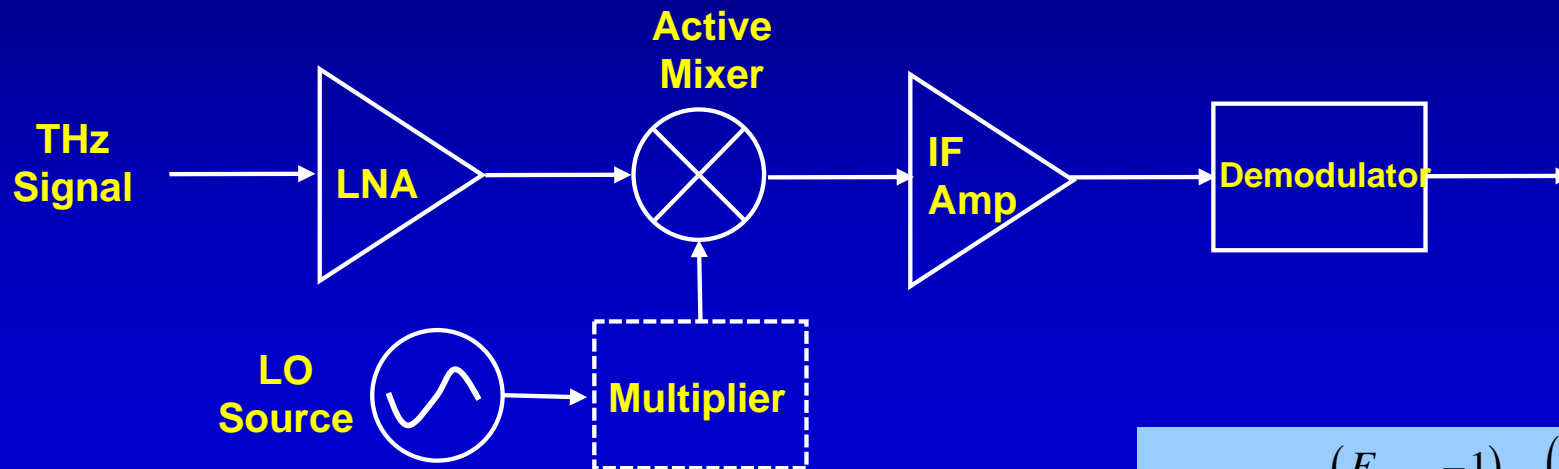


$$F = F_{LNA} + \frac{(F_{Mixer} - 1)}{G_{LNA}} + \frac{(F_{IFamp} - 1)}{G_{LNA} G_{Mixer}} + \dots$$

- Widely accepted architecture for low frequency receivers
 - Addition of LNA
 - Active mixer with gain or reduced loss
 - Integration-friendly LO
 - Enabled by transistor-based semiconductor technologies
 - Can this architecture be applied to THz receivers, too?

Semiconductor Technologies for THz

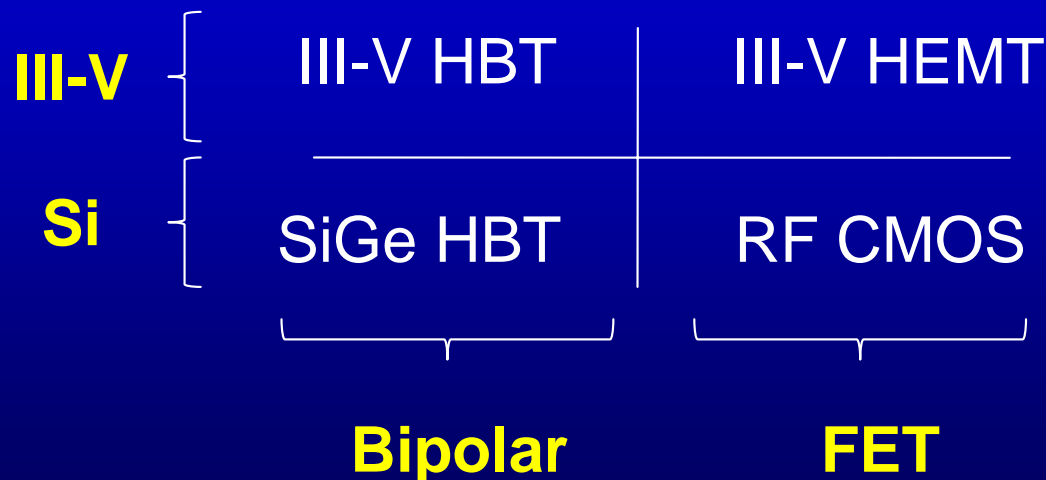- III-V technologies
 - HBT (heterojunction bipolar transistor) technologies
 - HEMT (high electron mobility transistor) technologies
- Si-based technologies
 - SiGe HBT technologies
 - RFCMOS technologies



Technology Comparison

GaAs/InP
HBT or HEMT

- Very high operation speed
- High cost
- Reliability issues


SiGe BiCMOS

- High operation speed
- CMOS-technology compatible
- High reliability
- Extra mask steps on base CMOS technology




CMOS

- Acceptable operation speed
- Low cost and high reliability
- Relatively low g_m
- Poor device matching

Operation Speed Trend of Technologies


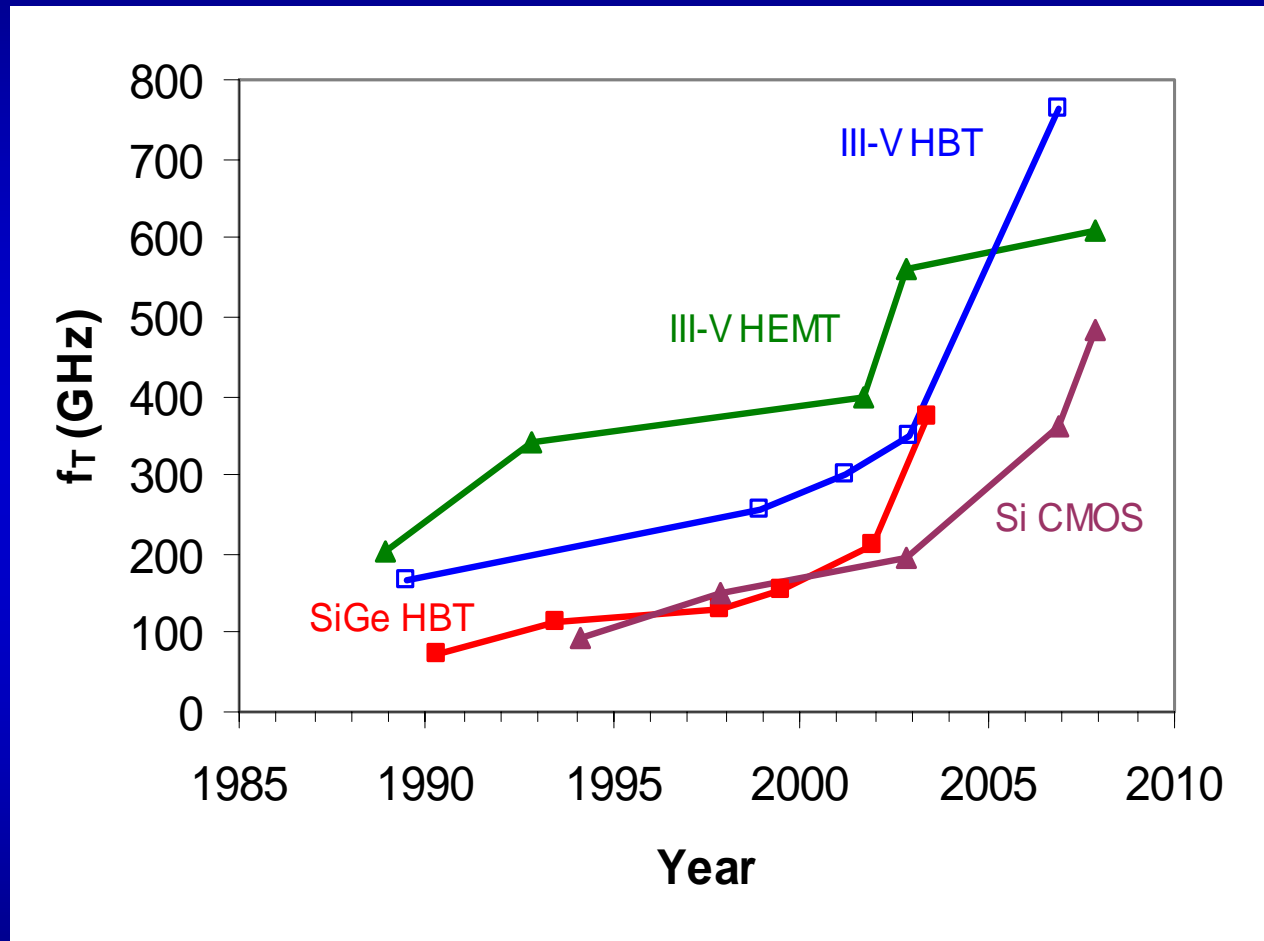


III-V HBT Record Performance

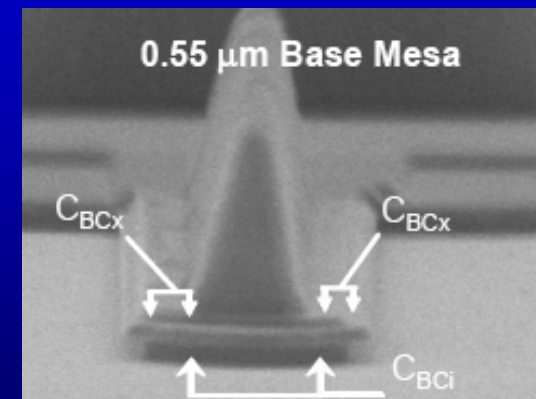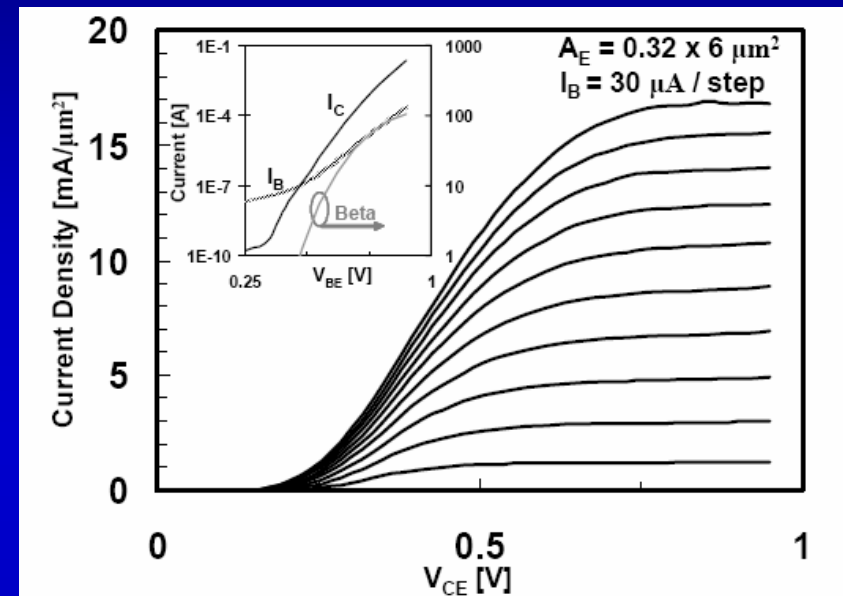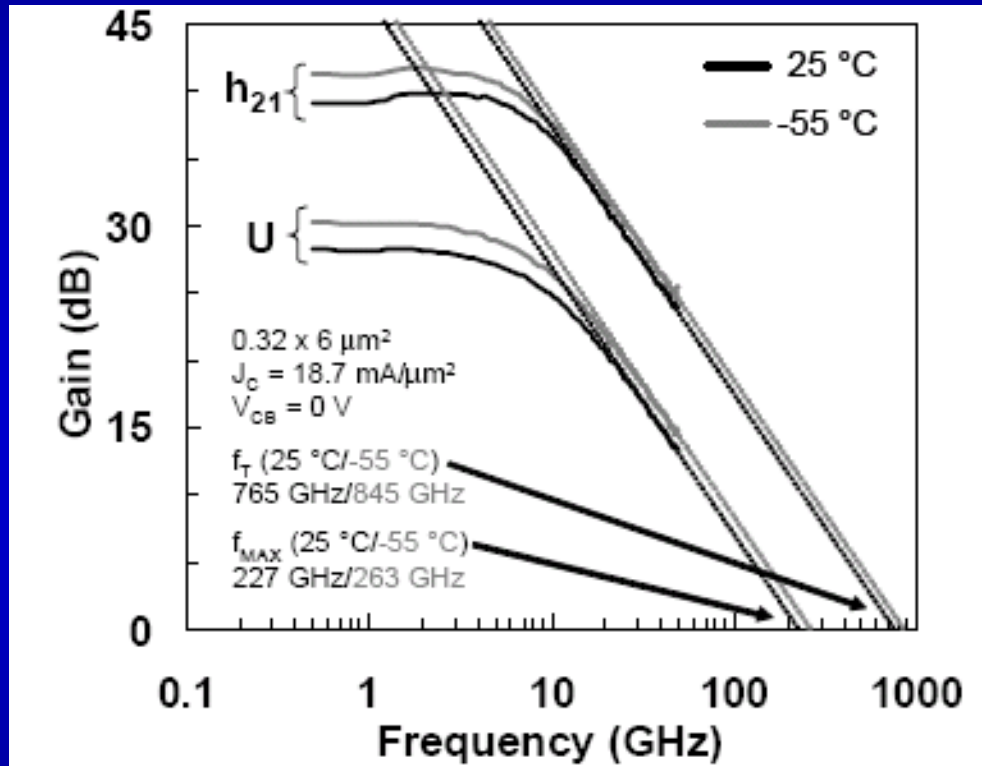




- UIUC
- Peak $f_T = 765 \text{ GHz}$ at 25C
- Peak $f_T = 845 \text{ GHz}$ at -55C

III-V HBT Performance Issues

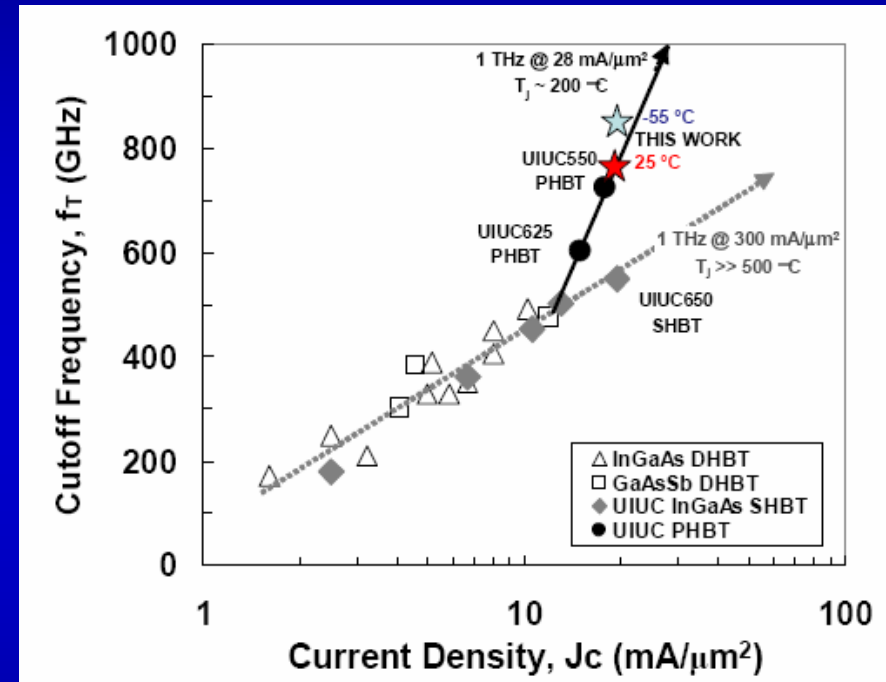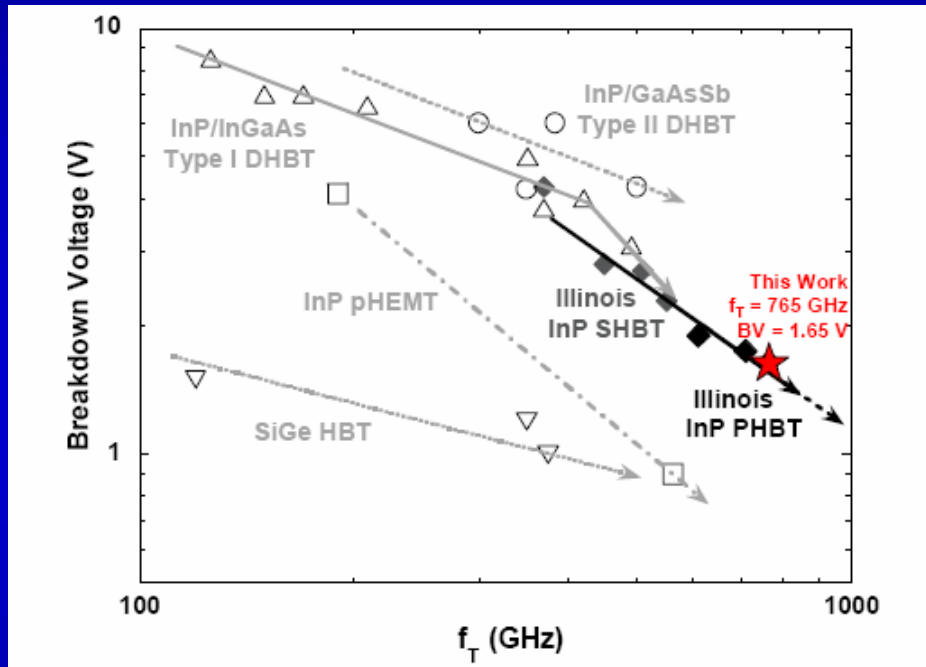



- Issues with increasing operation frequency
 - Reduction in breakdown voltage \rightarrow Limits safe operation region
 - Increase in collector current density \rightarrow Influences reliability

HEMT Record Performance

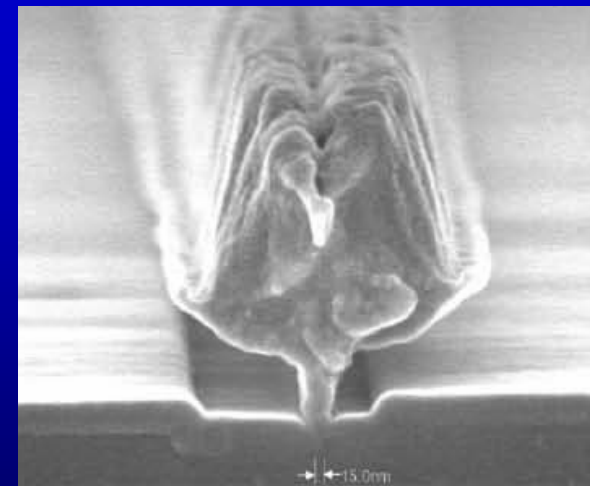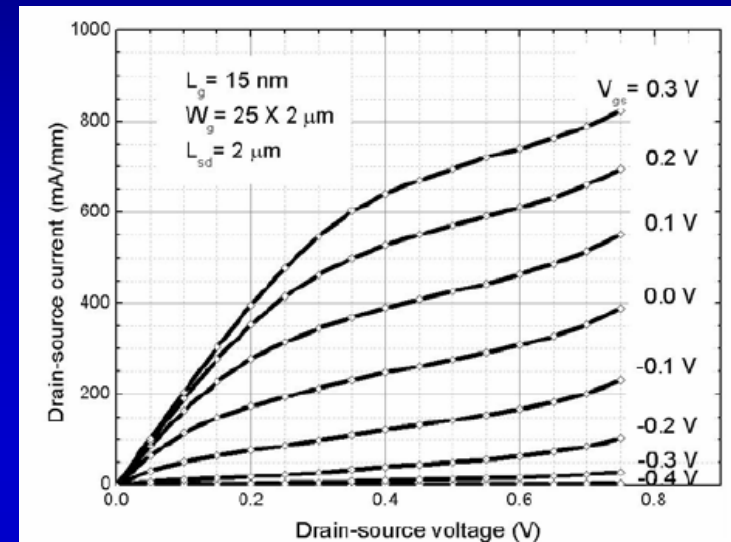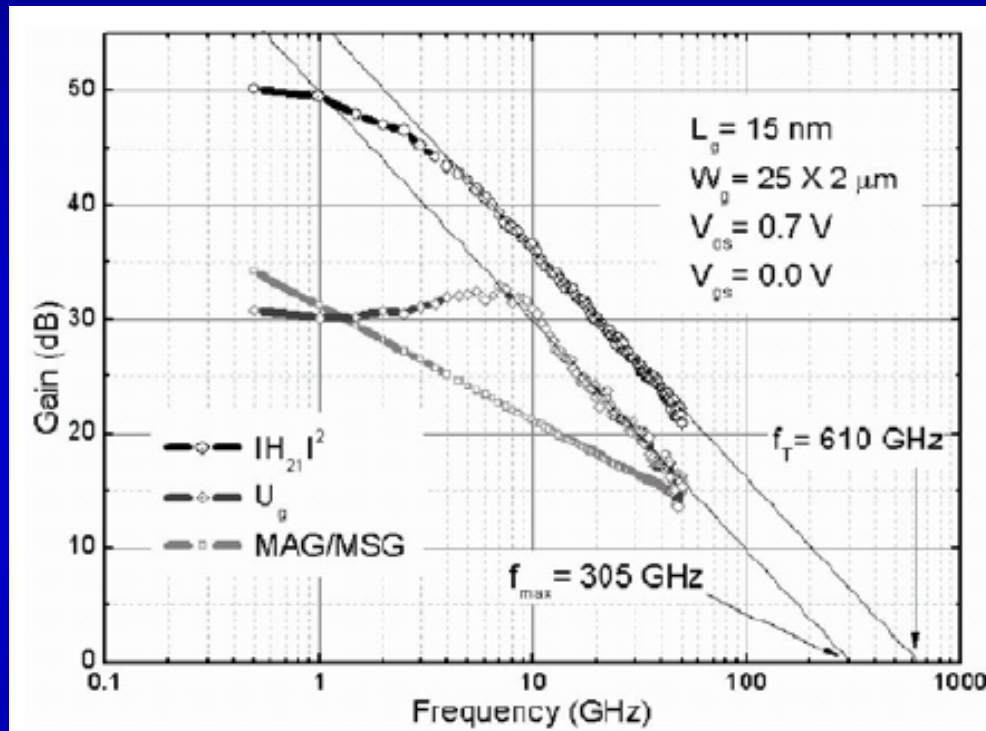


- Seoul National Univ.
- 15 nm gate length InP HEMT
- Peak $f_T / f_{max} = 610/305 \text{ GHz}$

SiGe HBT Record Performance

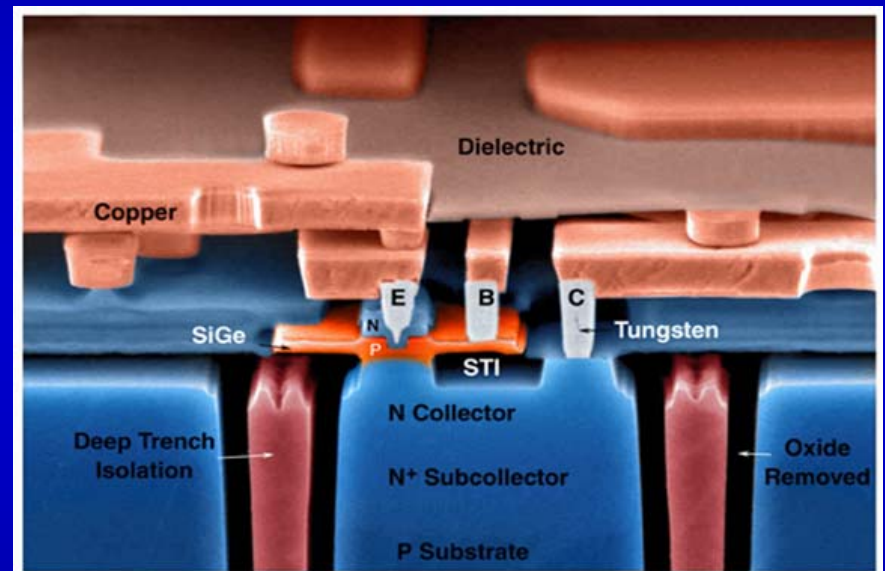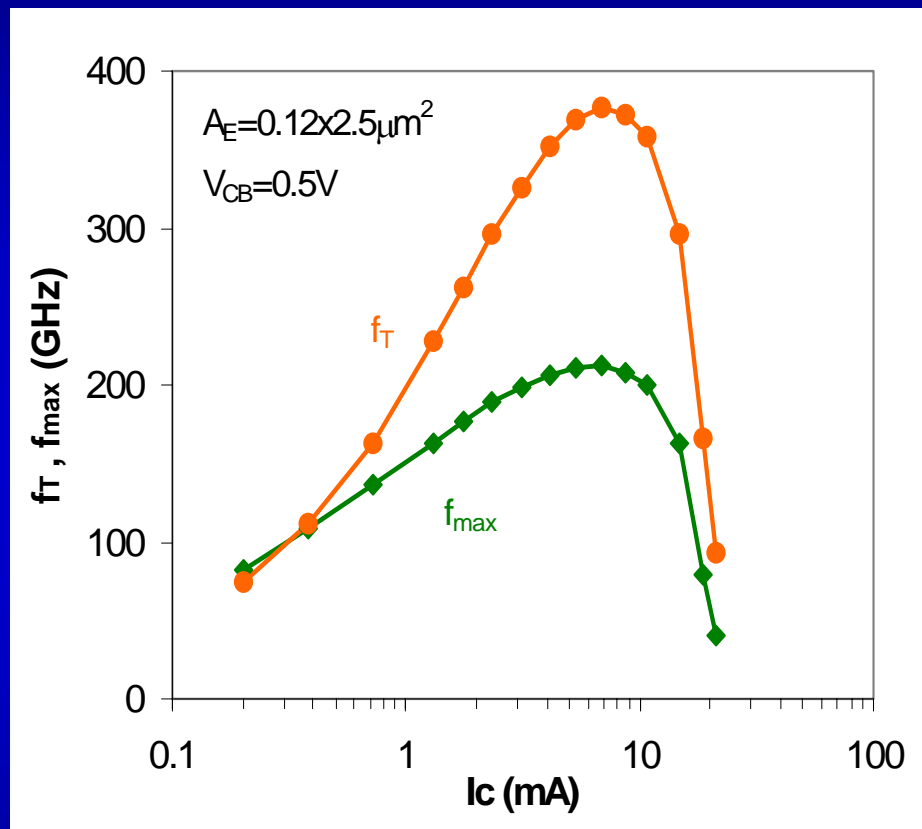

- IBM
- 0.12 μm SiGe HBT
- Peak $f_T / f_{max} = 375/210$ GHz


SiGe HBT Performance Trend

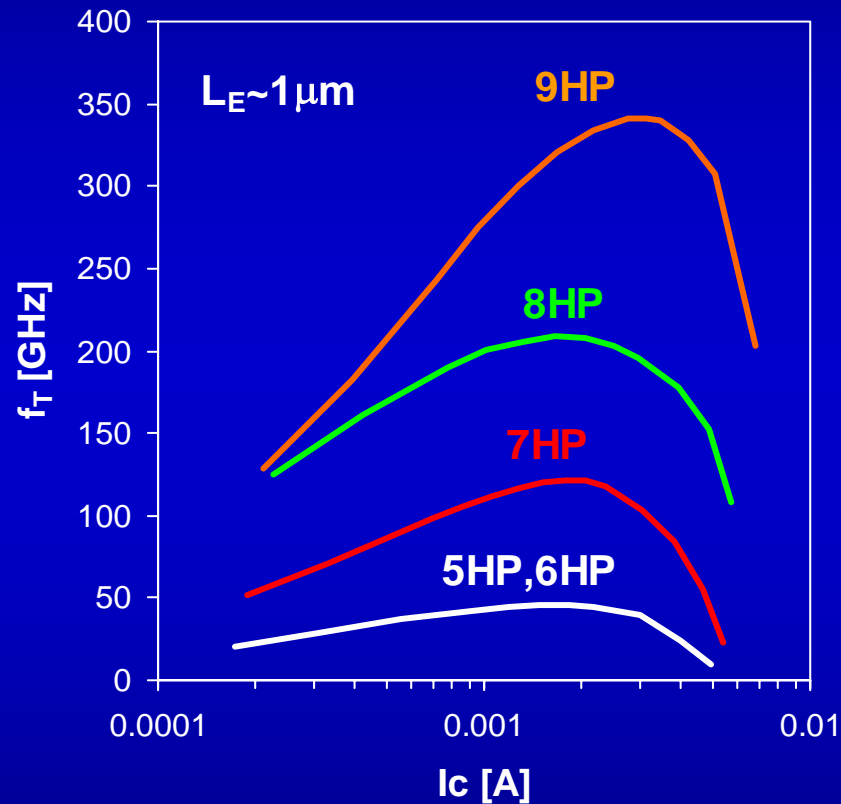



	5HP 6HP	7HP	8HP	9HP
f_T [GHz]	47	120	210	350
f_{max} [GHz]	85	150	285	300
$J_{C,p}$ [mA/ μm^2]	~1.5	~8	~12	~19
BV_{CEO} [V]	3.4	1.8	1.7	1.7
BV_{CBO} [V]	10.5	6.5	5.5	5.6
Beta	100	300	300	650

- Trend of IBM SiGe HBTs

SiGe HBT f_T and f_{max}

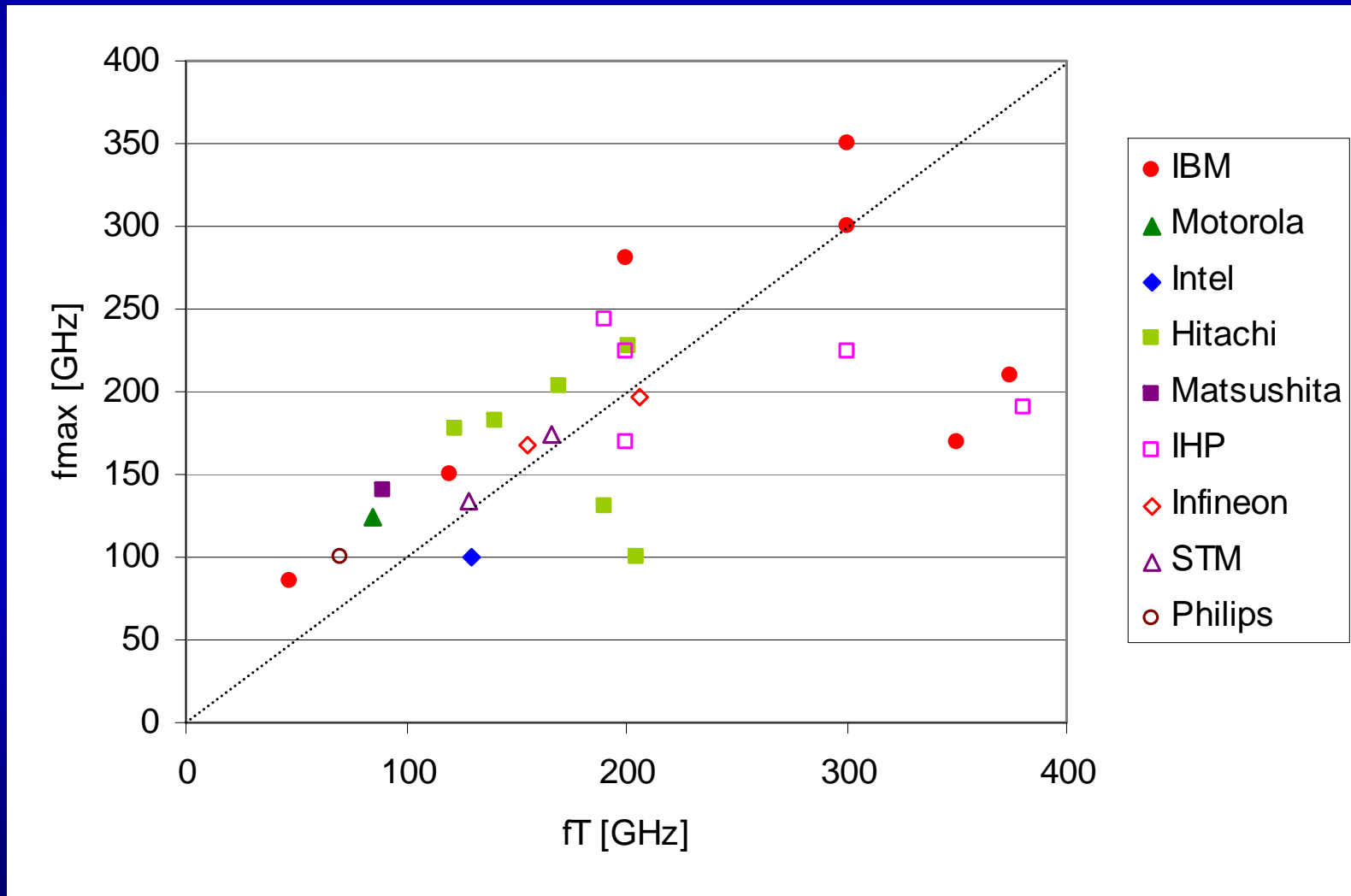



RFCMOS Record Performance (I)

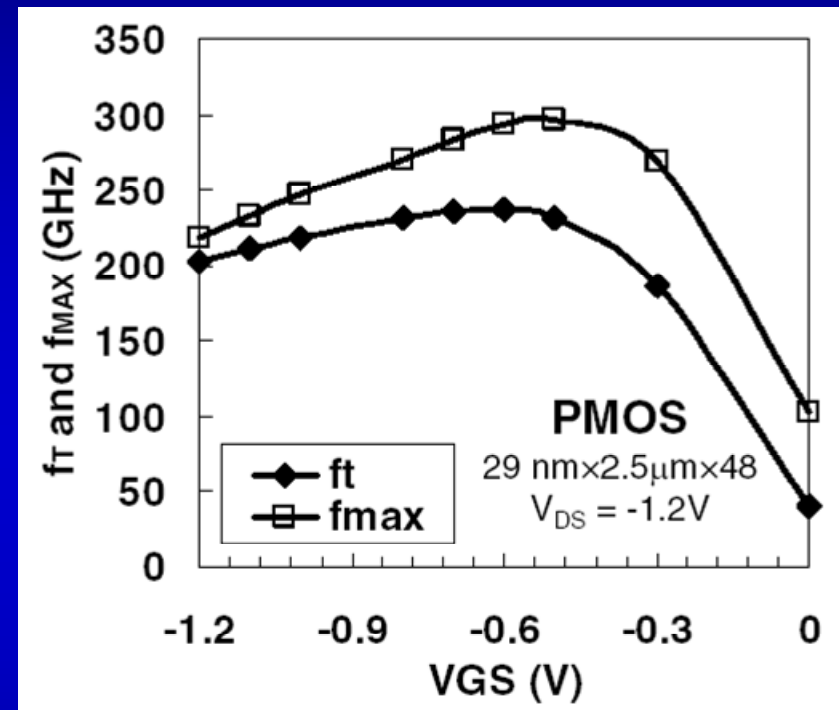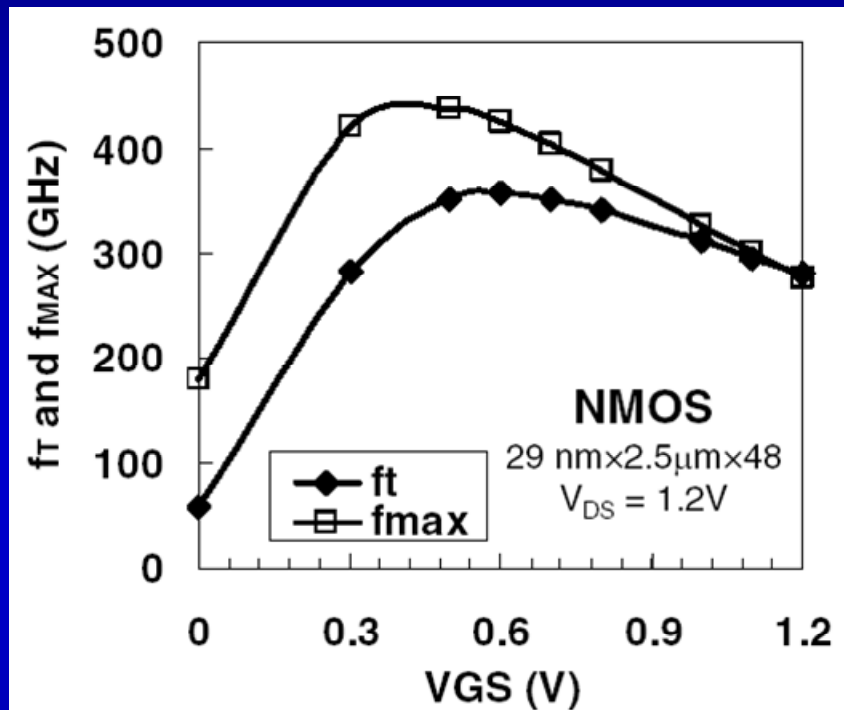

- 65 nm SOI NFET ($L_{\text{poly}}=29 \text{ nm}$)
- Peak $f_T / f_{\text{max}} = 360/420 \text{ GHz}$

- 65 nm SOI PFET
- Peak $f_T / f_{\text{max}} = 238/295 \text{ GHz}$

RFCMOS Record Performance (II)

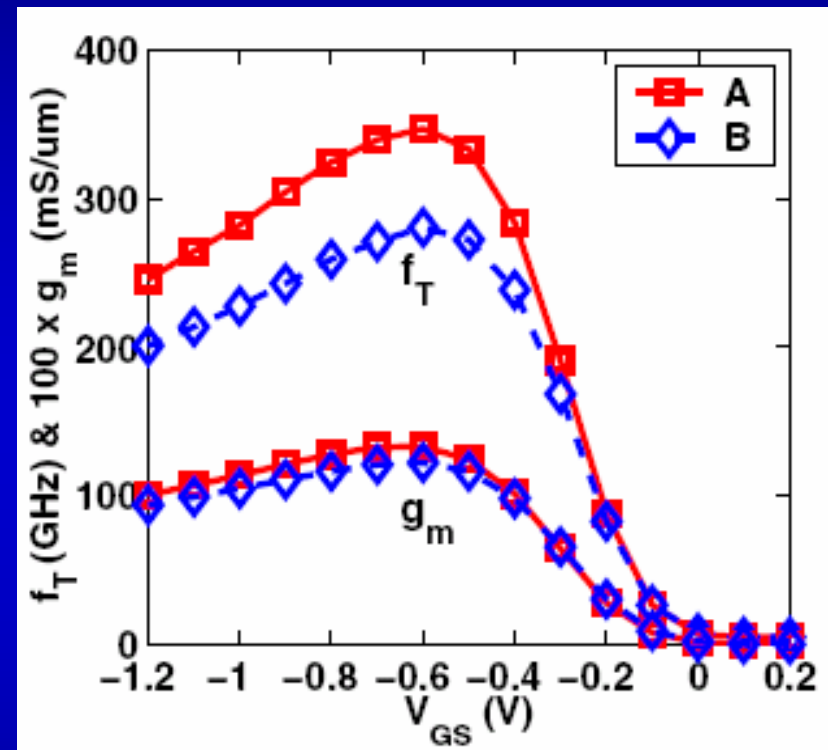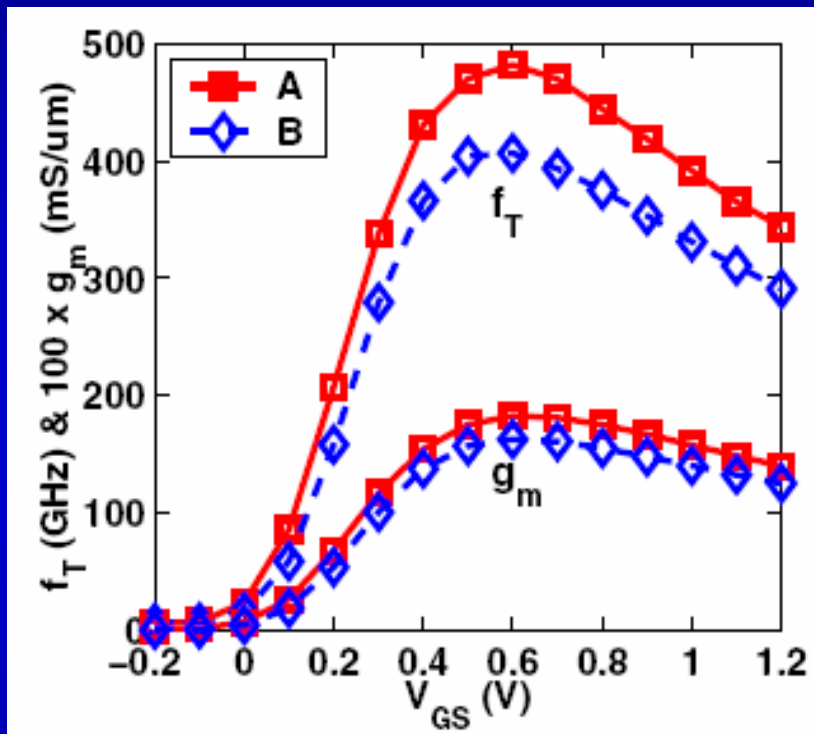

- NFET: 45 nm SOI ($L_{poly}=29$ nm)
- Peak $f_T = 485$ GHz

- PFET: 45 nm SOI ($L_{poly}=31$ nm)
- Peak $f_T = 345$ GHz

A: Relaxed poly pitch, B: Minimum poly pitch

ITRS Roadmap 2007 for RFCMOS


Near-term

Year of Production	2007	2008	2009	2010	2011	2012	2013	2014	2015
DRAM $\frac{1}{2}$ Pitch (nm) (contacted)	65	57	50	45	40	35	32	28	25
<i>Performance RF/Analog [1]</i>									
Supply voltage (V) [2]	1.2	1.1	1.1	1	1	1	1	0.95	0.85
T_{ox} (nm) [2]	2	1.9	1.6	1.5	1.4	1.3	1.2	1.1	1.2
Gate Length (nm) [2]	53	45	37	32	28	25	22	20	18
g_m/g_{ds} at $5 \cdot L_{min-digital}$ [3]	32	30	30	30	30	30	30	30	30
1/f-noise ($\mu V^2 \cdot \mu m^2/Hz$) [4]	160	140	100	90	80	70	60	50	60
σV_{th} matching (mV $\cdot\mu m$) [5]	6	6	5	5	5	5	5	5	5
I_{ds} ($\mu A/\mu m$) [6]	13	11	9	8	7	6	6	5	4
Peak F_t (GHz) [7]	170	200	240	280	320	360	400	440	490
Peak F_{max} (GHz) [8]	200	240	290	340	390	440	510	560	630
NF _{min} (dB) [9]	0.25	0.22	0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2


Long-term

Year of Production	2016	2017	2018	2019	2020	2021	2022
DRAM $\frac{1}{2}$ Pitch (nm) (contacted)	22	20	18	16	14	13	11
<i>Performance RF/Analog [1]</i>							
Supply voltage (V) [2]	0.8	0.8	0.8	0.8	0.75	0.75	0.7
T_{ox} (nm) [2]	1.1	1.1	1	1	0.9	0.9	0.8
Gate Length (nm) [2]	16	14	13	12	11	10	10
g_m/g_{ds} at $5 \cdot L_{min-digital}$ [3]	30	30	30	30	30	30	30
1/f-noise ($\mu V^2 \cdot \mu m^2/Hz$) [4]	50	50	40	40	30	30	30
σV_{th} matching (mV $\cdot\mu m$) [5]	4	4	4	4	3	4	5
I_{ds} ($\mu A/\mu m$) [6]	4	3	3	3	2	2	2
Peak F_t (GHz) [7]	550	630	670	730	790	870	870
Peak F_{max} (GHz) [8]	710	820	880	960	1050	1160	1160
NF _{min} (dB) [9]	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2


320 GHz InP HEMT Amplifier

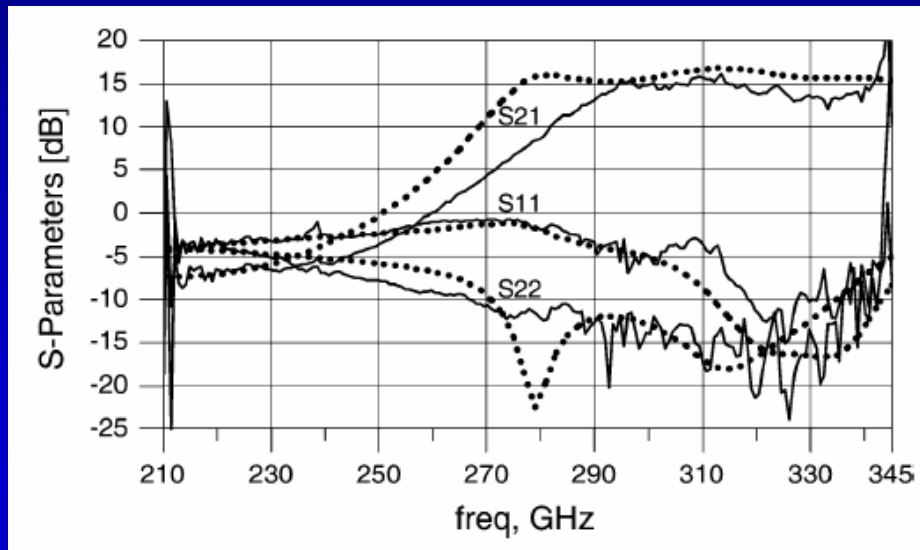


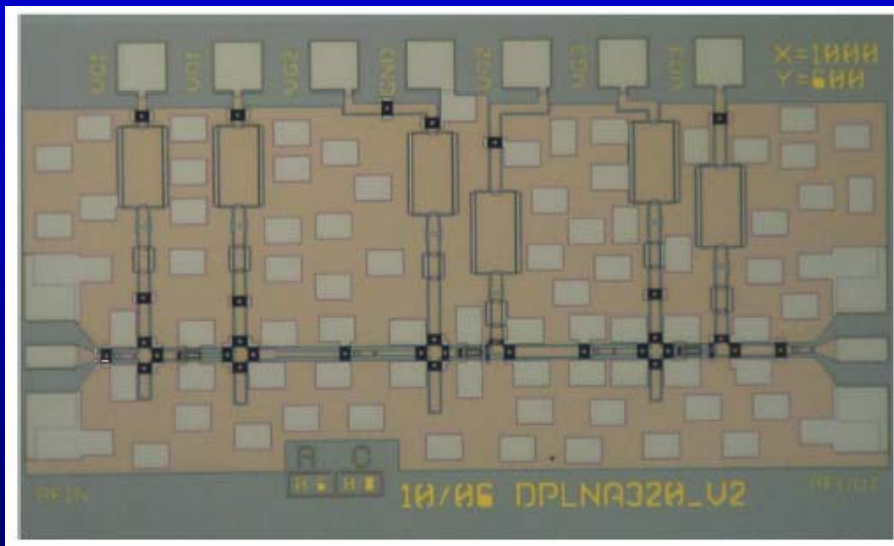
- NGC
- 35 nm NGC InP HEMT
- 3 stage
- $P_{\text{Diss}} = 43 \text{ mW}$
- Gain = 13-15 dB for 295-340 GHz




324 GHz InP HBT Amplifier

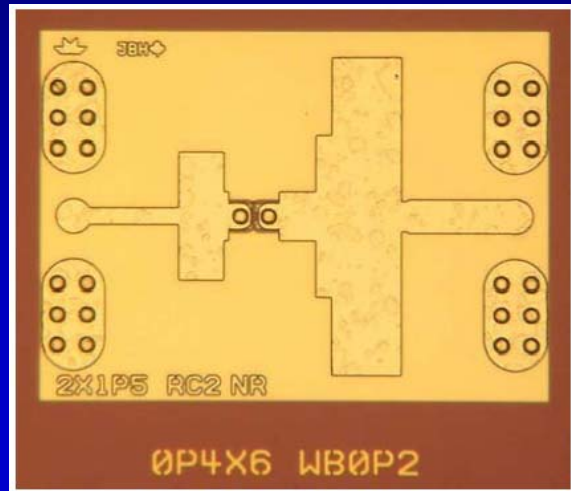

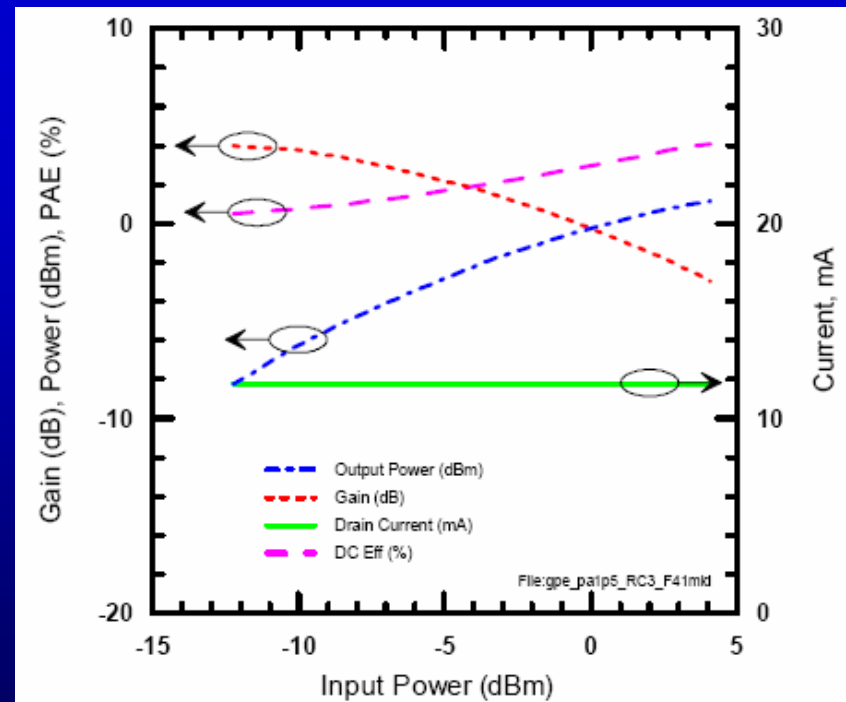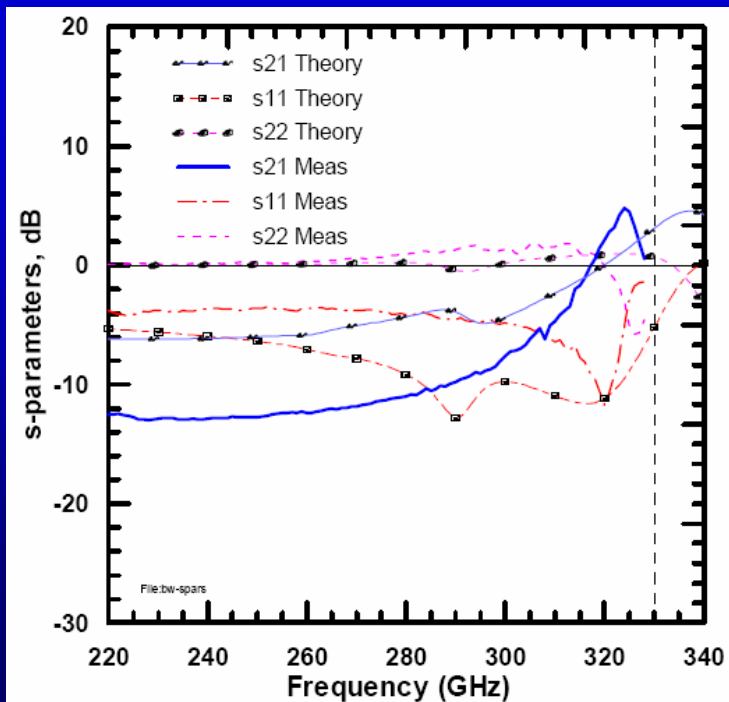
- Teledyne
- 250 nm Teledyne InP HBT
- Single stage common base
- Gain = 4.8 dB at 324 GHz
- Saturated $P_{out} = 1.13$ dBm




220 GHz GaAs MHEMT LNA

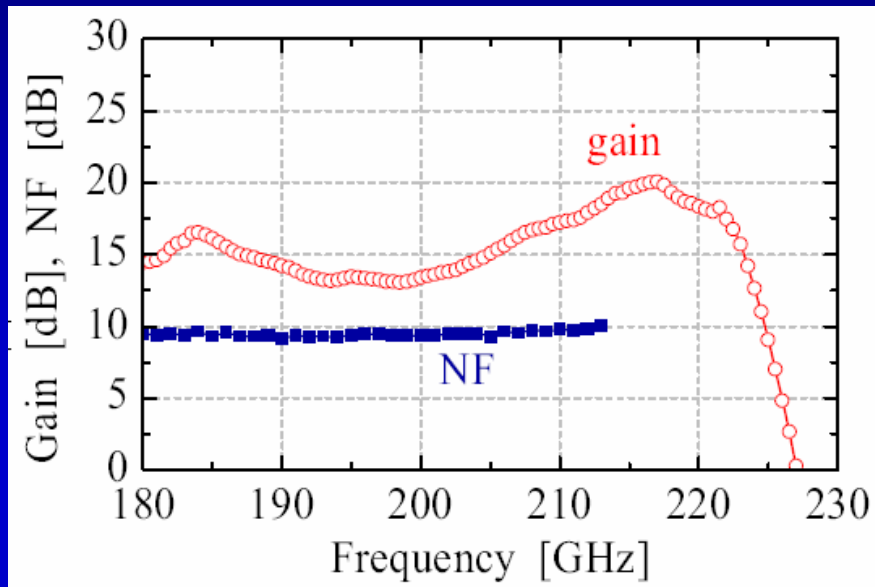


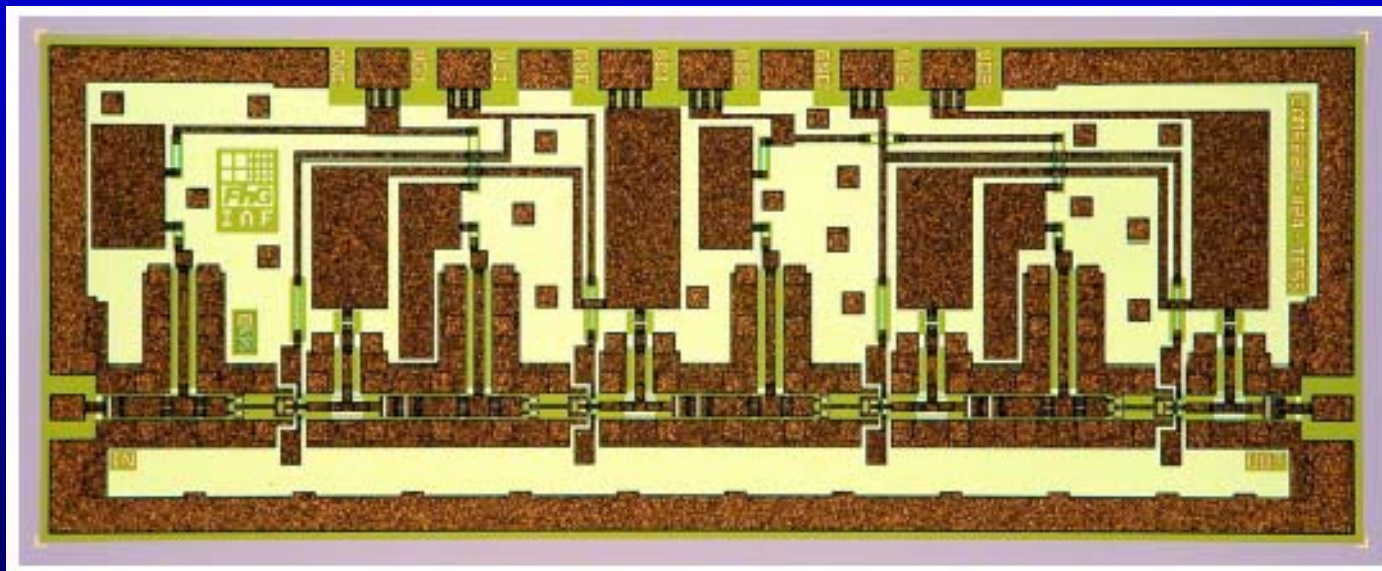
- Franhofer
- 0.1 um Franhofer GaAs mHEMT
- 4 stage cascode
- Peak gain = ~20 dB
- NF = 9.4 dB up to 213 GHz




140 GHz SiGe HBT Amplifier

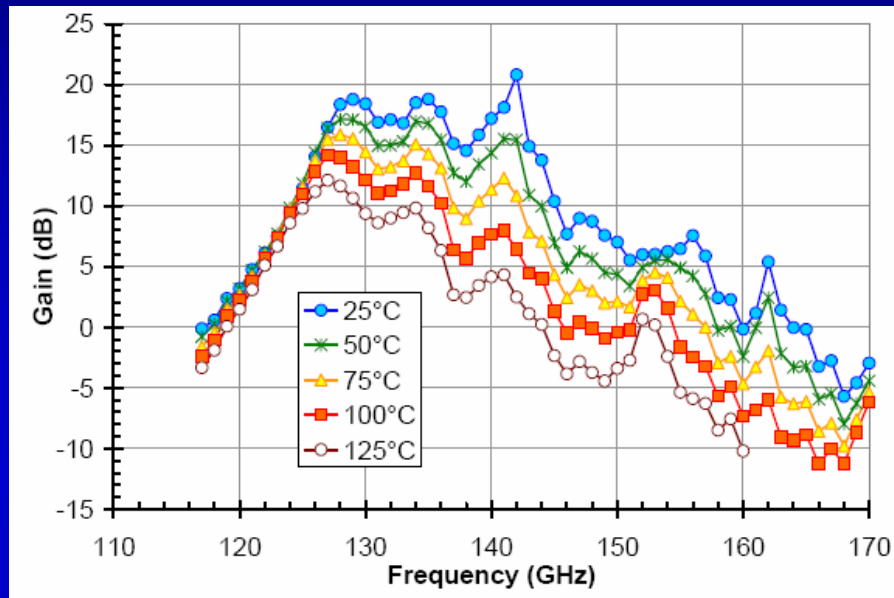

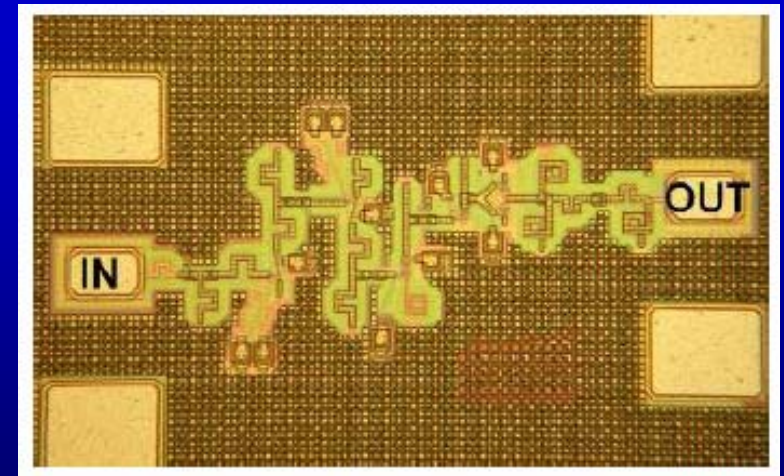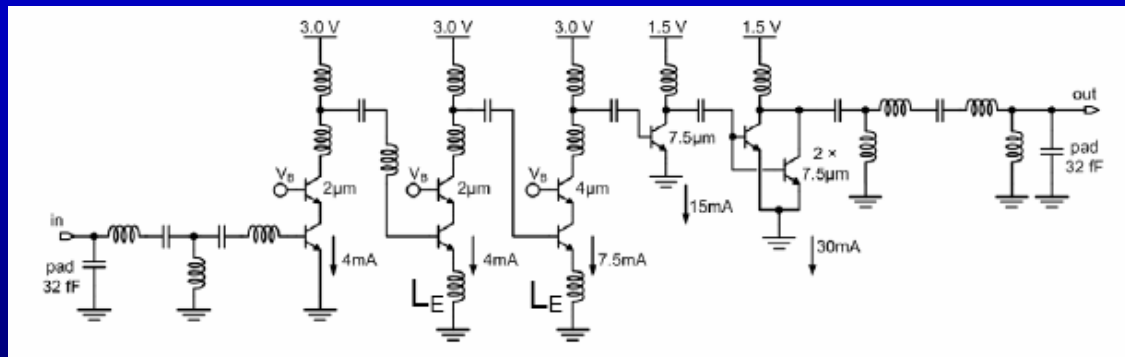
- Univ. of Toronto
- STM SiGe BiCMOS
- 5 stage cascode
- $P_{\text{Diss}} = 112 \text{ mW}$
- Gain = 17 dB at 140 GHz




Accumulated Performance: Amplifiers

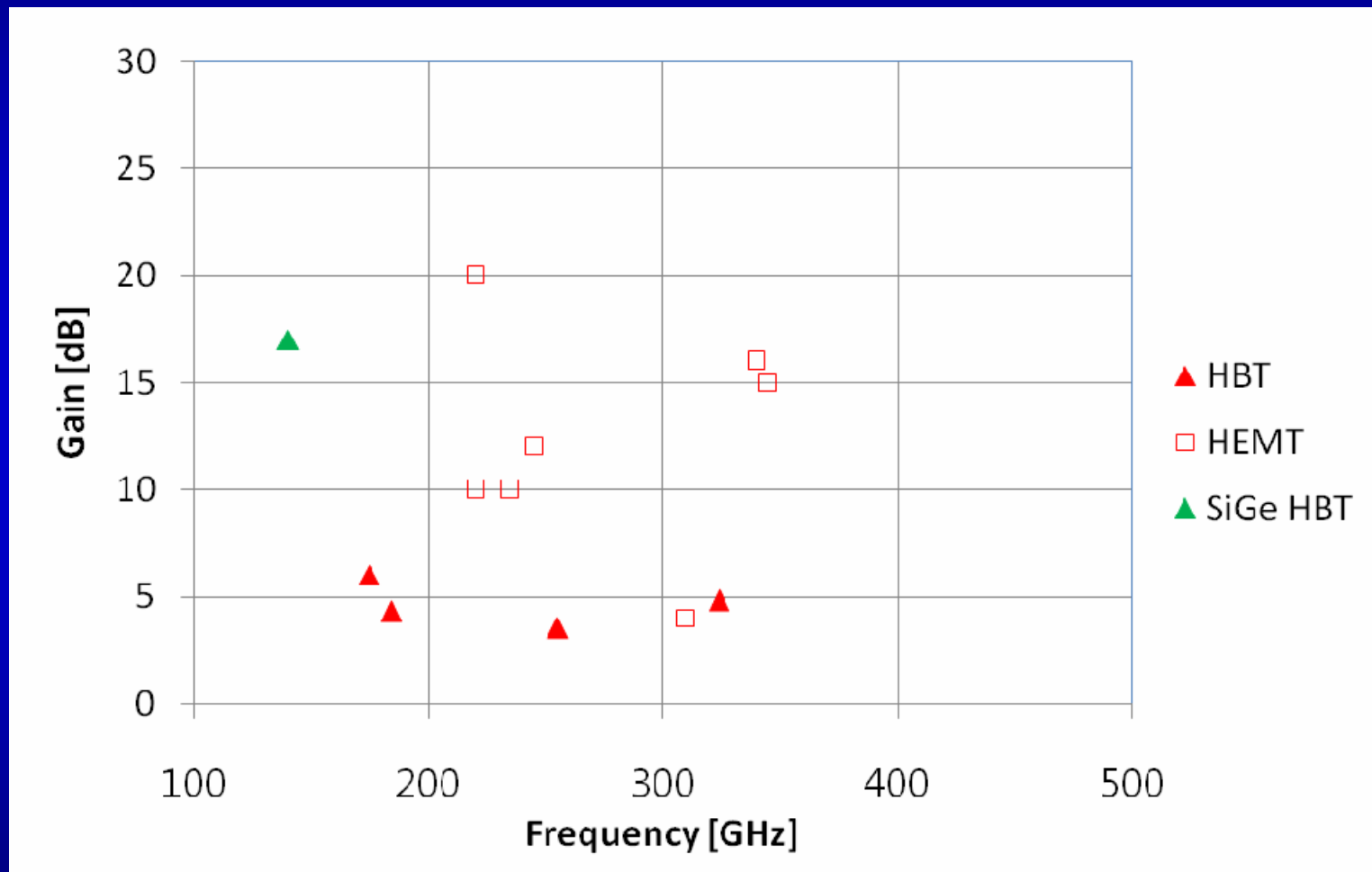

346 GHz InP HEMT Fundamental Oscillator

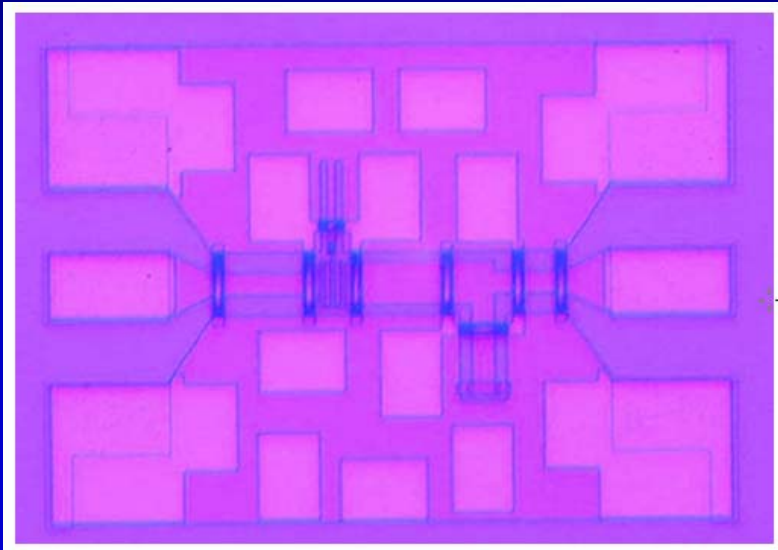


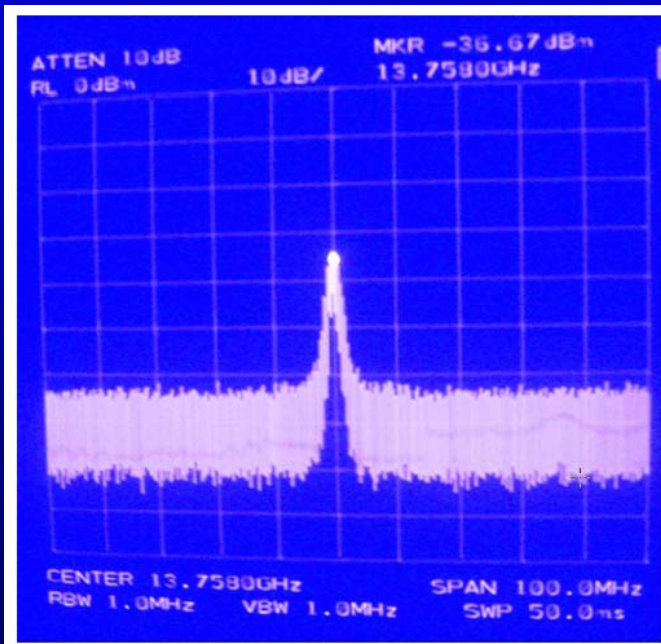- NGC
- 35 nm NGC InP HEMT
- DC power = 11.7 mW
- Output power = -16 dBm at 346 GHz





Frequency of Oscillation (GHz)	Vds (V)	Ids (mA)	Measured Output Power (μ W)	DC to RF Efficiency (%)
254	1.3	9	158	1.35
314	1.2	6	46	0.64
346	1.3	9	25	0.21


278 GHz SiGe HBT Push-Push VCO

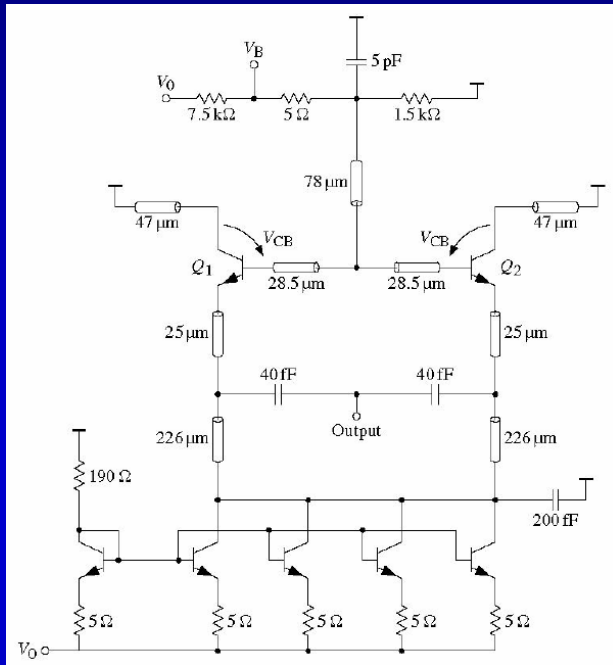

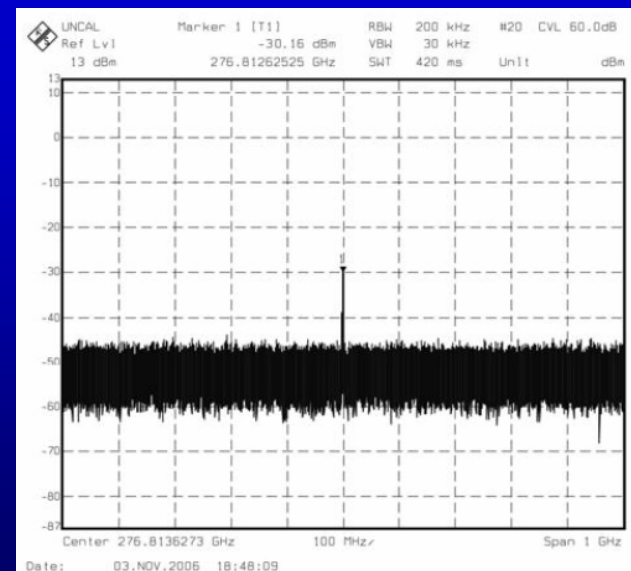
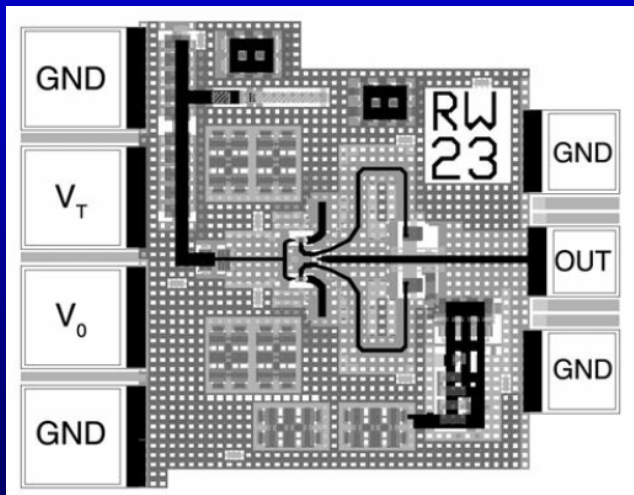
- Technische Univ. Munchen
- Infineon 200 GHz SiGe HBT Technology
- Tuning range: 275.5 - 279.6 GHz
- Output power = -30 dBm at 277 GHz
- DC power = 132 mW




410 GHz RFCMOS Push-Push VCO

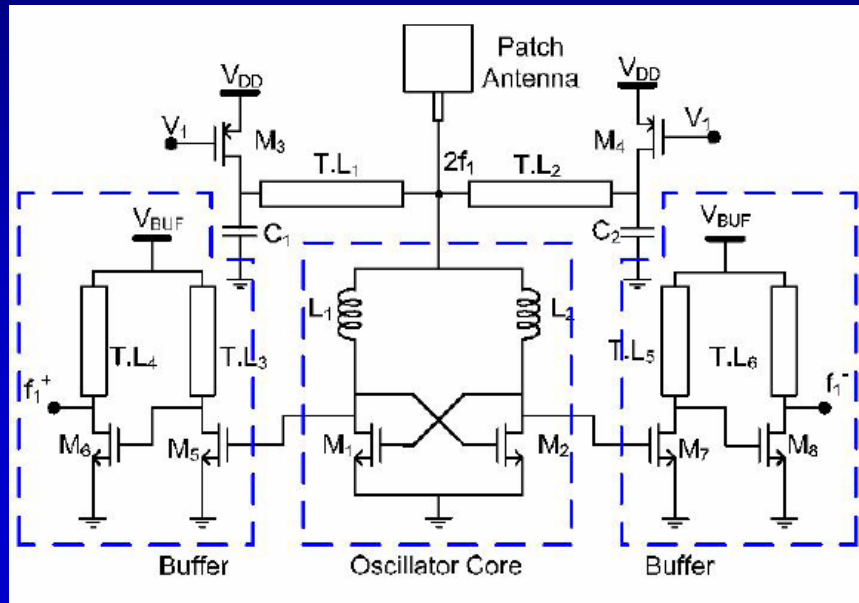

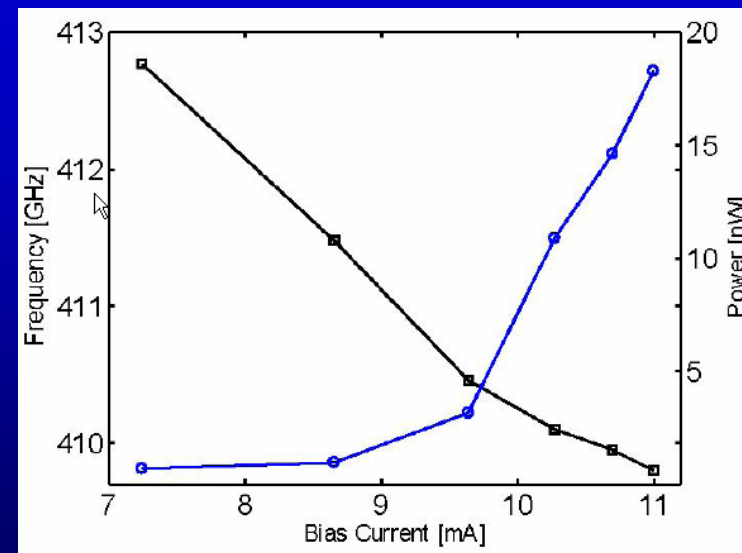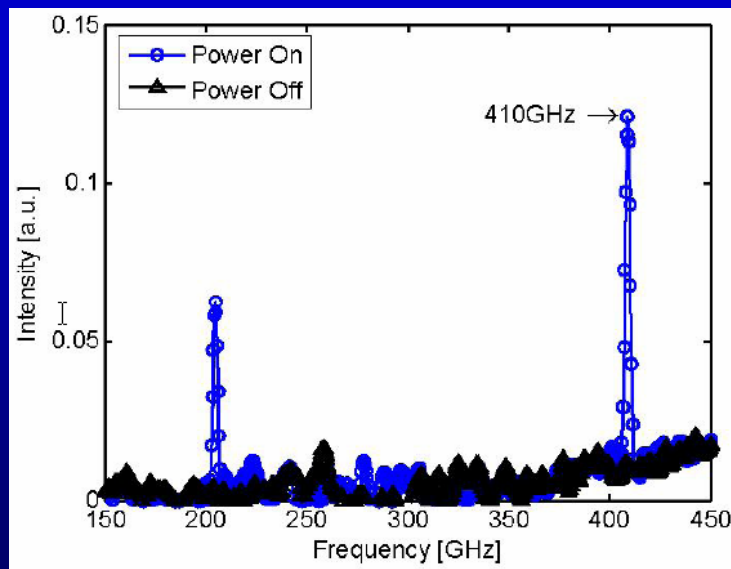
- Univ. of Florida
- 45 nm RFCMOS
- Output power = -47 dBm at 410 GHz
- DC power = 16.5 mW




Accumulated Performance: Oscillators (I)

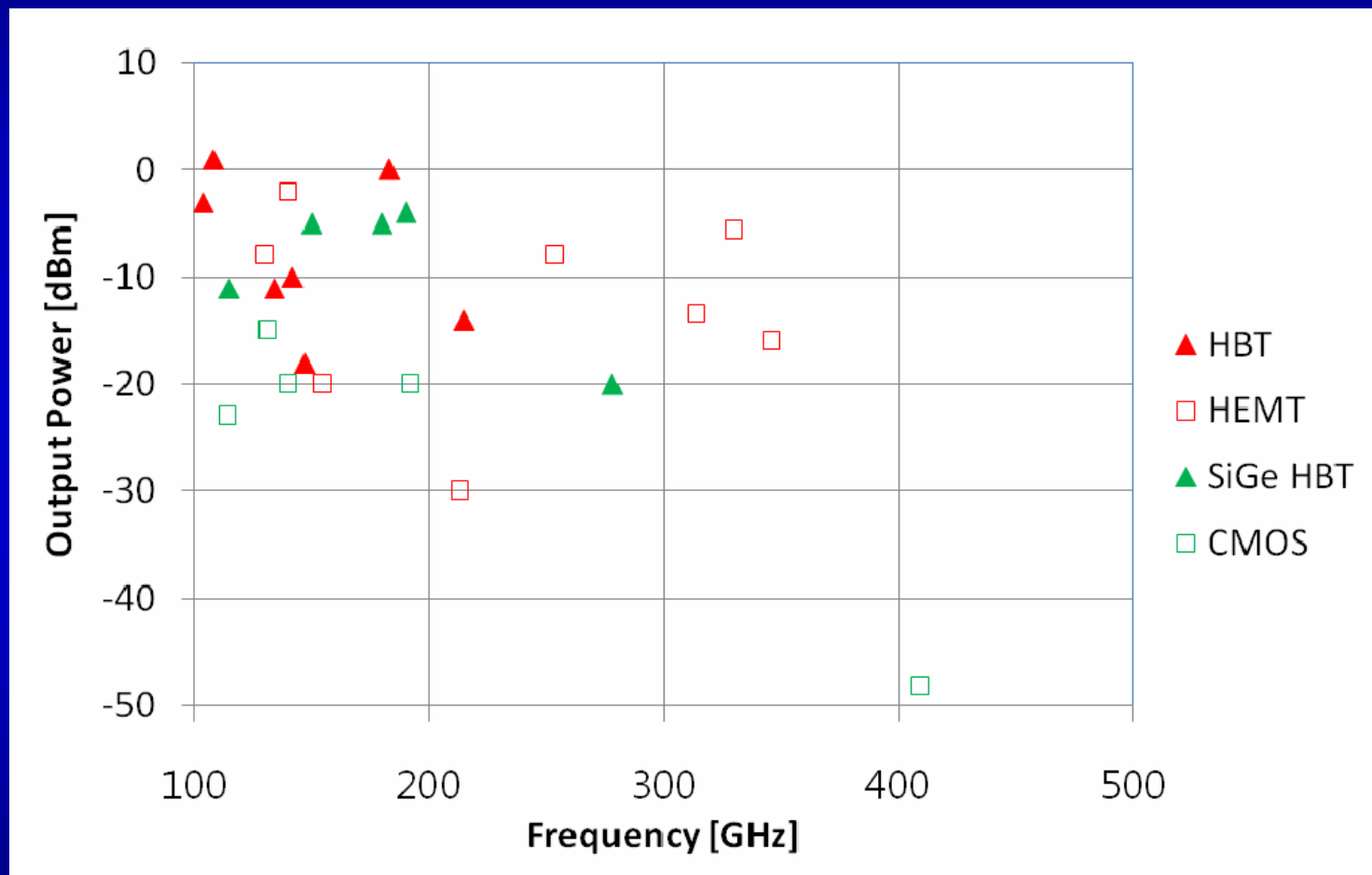



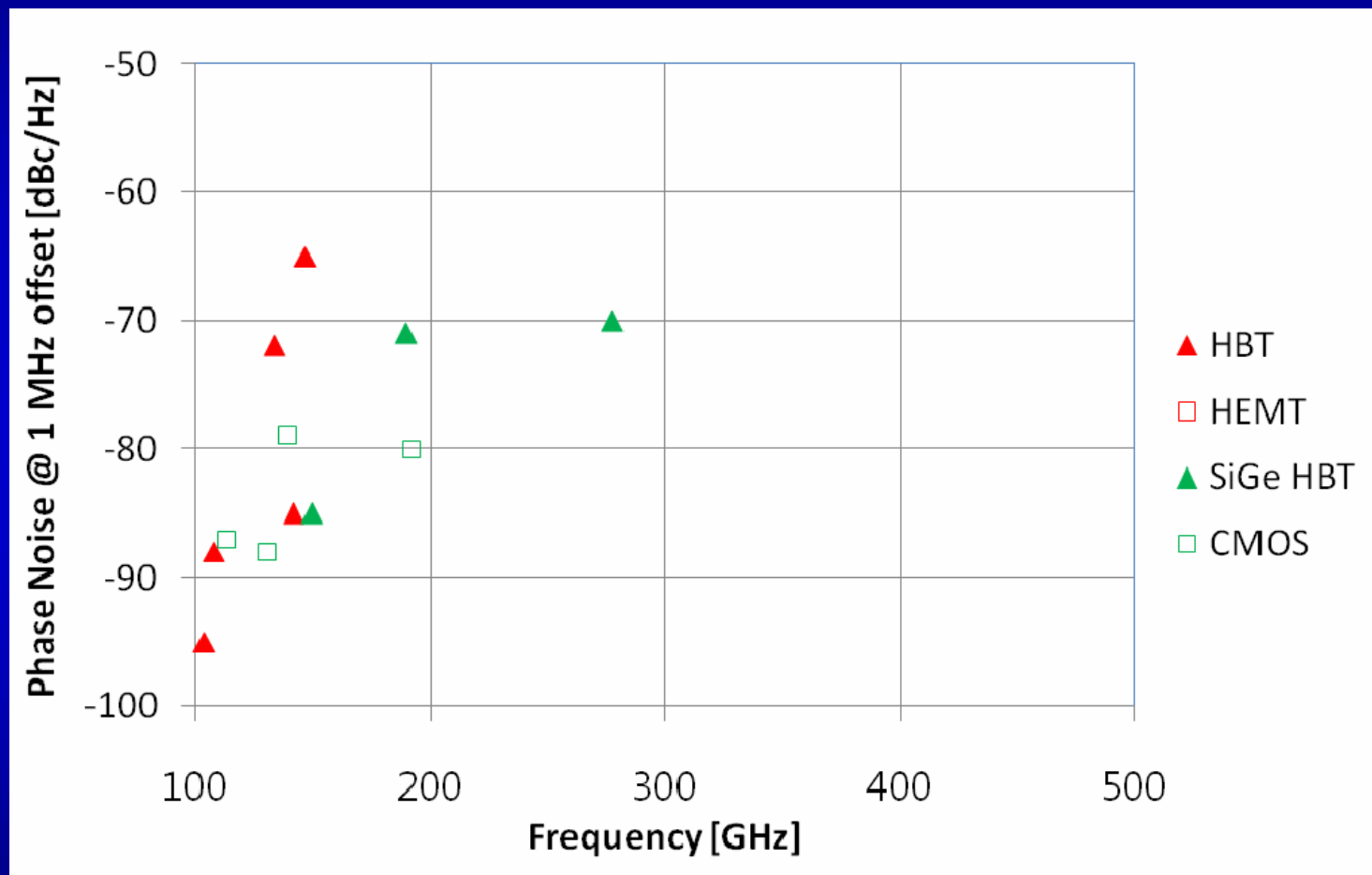
Accumulated Performance: Oscillators (II)




220 GHz MHEMT Active Mixer

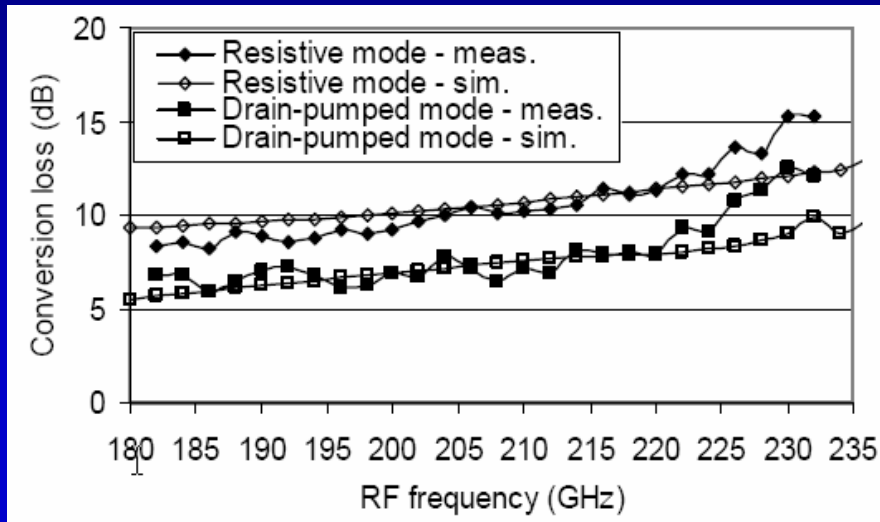

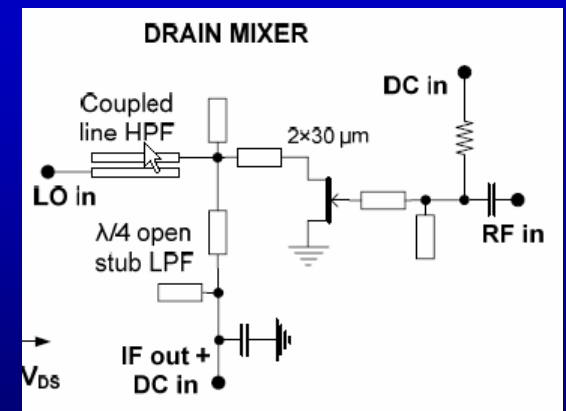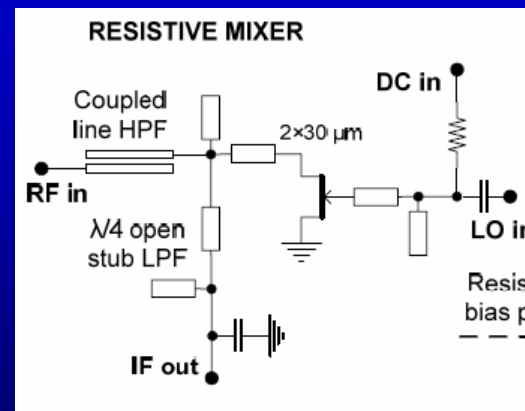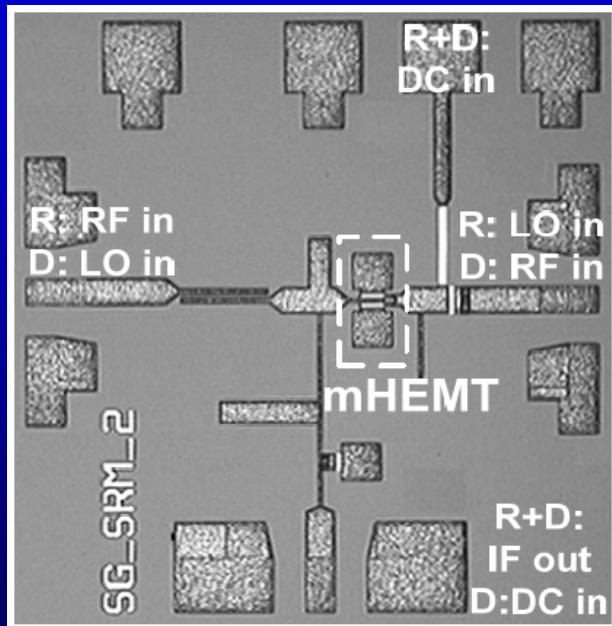- Chalmers University
- 0.1 um GaAs MHEMT
- Conversion loss = ~12 dB for resistive mixer mode
- Conversion loss = ~8 dB for drain mixer mode



Accumulated Performance: Active Mixers

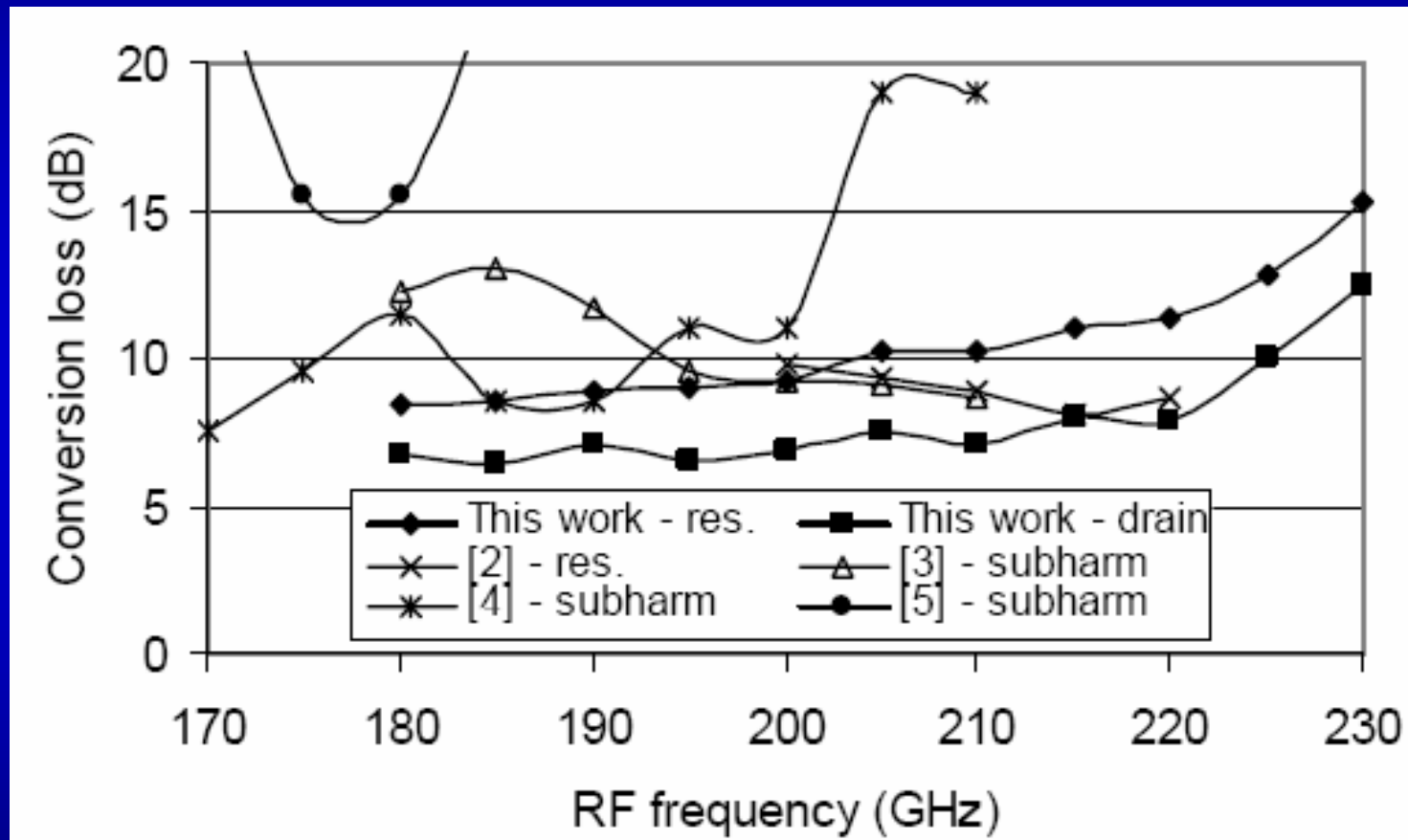

Summary

- Current status of semiconductor technologies
 - III-V HBT: $f_T \sim 785$ GHz
 - III-V HEMT: $f_T \sim 610$ GHz
 - SiGe HBT: $f_T \sim 375$ GHz
 - RFCMOS: $f_T \sim 485$ GHz
 - Current status of circuits
 - Amplifiers: up to 345 GHz (15 dB gain)
 - Oscillators: up to 410 GHz for push-push, 346 GHz for fundamental
 - Active mixers: up to ~ 220 GHz with conversion loss ~ 8 dB
- Transistor-based THz front-end highly promising